

Notes

PHYSICS 11

OHM'S LAW

$$R = \frac{V}{I} \quad \text{or} \quad V = IR \quad \text{or} \quad I = \frac{V}{R}$$

where R is resistance measured in Ohms [Ω]
V is voltage measured in Volts [V]
and I is electric current measured in Amperes [A]

RESISTANCE

$$R = \rho \frac{L}{A}$$

where ρ is resistivity of the material measured in Ohm meter [$\Omega \cdot \text{m}$]
A is the cross-sectional area of the conductor measured in meter squared [m^2]
and L is the length of the conductor measured in meters [m]

ELECTRIC POWER


$$P = IV = I^2R$$

where P is power measured in Watts [W]
I is electric current measured in Amperes [A]
V is voltage measured in Volts [V]
and R is resistance measured in Ohms [Ω]

RESISTORS CONNECTED IN SERIES

- Equivalent (total) resistance in a circuit with resistors in series is the sum of all individual resistances.
- Same current goes through every resistor.
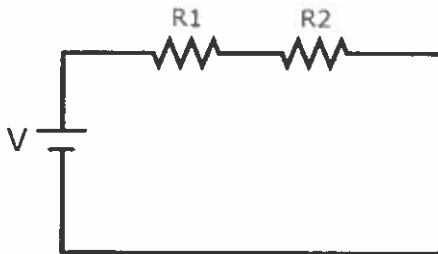
$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$$



RESISTORS CONNECTED IN PARALLEL

- Equivalent (total) resistance in a circuit with resistors in parallel is calculated by finding the sum of reciprocal values of all resistors followed by reciprocating that sum.


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}}$$

$$\bullet I_1 = \frac{V_1}{R_1}$$

➤ Same voltage is applied across each resistor.
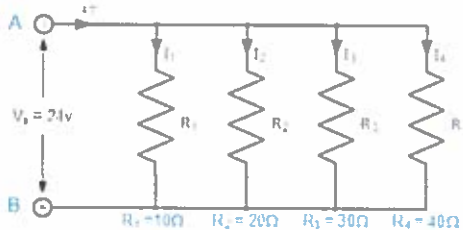
$$\rightarrow \frac{24}{10} = \underline{2.4A}$$



$$\bullet I_2 = \frac{24}{20} = \underline{1.2A}$$

$$\bullet I_4 = \frac{24}{40} = 0.6A = \frac{24}{40}$$

$$\bullet I_3 = \frac{24}{30} = \underline{0.8A}$$

$$\bullet I_{TOT} = \frac{V_B}{R_{eq}}$$

$$= 5.0A$$

$$\bullet \frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{20} + \frac{1}{30} + \frac{1}{40}$$

$$\frac{1}{R_{eq}} = \frac{12+6+4+3}{120} = \frac{25}{120}$$

$$\rightarrow R_{eq} = \frac{120}{25} = \underline{\underline{4.8\Omega}}$$

$$\bullet V_1 = V_2 = V_3 = V_4 = V_{battery} = \underline{24V}$$


$$\bullet I_{TOT} = I_1 + I_2 + I_3 + I_4$$

RESISTORS CONNECTED IN SERIES AND IN PARALLEL

➤ Most circuits have resistors wired in series as well as in parallel

Example : Find the equivalent resistance in the circuit below. If the battery provides 12.0 V of voltage, what is the current through the 10Ω resistor?

$$R_{eq} = ? [\Omega]$$

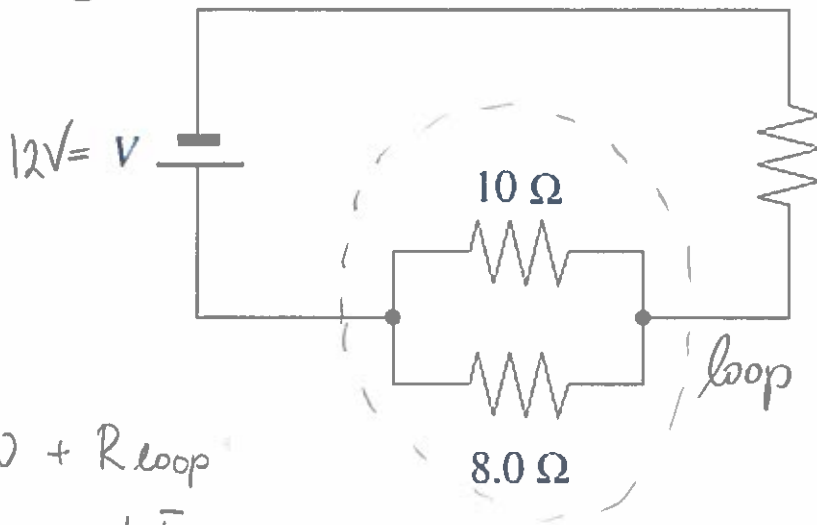

$$R_{loop} :$$

$$\begin{aligned} \frac{1}{R_{loop}} &= \frac{1}{10} + \frac{1}{80} \\ &= \frac{4 + 5}{40} \\ &= \frac{9}{40} \end{aligned}$$

$$\rightarrow R_{loop} = \frac{40}{9} = 4.\bar{4} \Omega$$

$$\begin{aligned} R_{eq} &= 4.0 + R_{loop} \\ R_{eq} &= 4.0 + 4.\bar{4} \\ &= 8.\bar{4} \Omega \end{aligned}$$

∴ The equivalent resistance is 8.4Ω.

$$I_{10} = ? [A]$$

$$I_{TOT} = I_4 = \frac{V_B}{R_{eq}} = \frac{12}{8.\bar{4}} = 1.4211 A$$

$$\rightarrow I_{TOT} = I_{10} + I_8 \quad \text{AND} \quad V_{10} = V_8 = V_B - V_4 = 12 - (4.0)(1.4211) = 6.3156 V$$

$$\begin{aligned} I_{10} &= \frac{V_{10}}{10} \\ &= \frac{6.3156}{10} \\ &= 0.63156 A \end{aligned}$$

∴ The current through the 10Ω resistor is 6.3 × 10⁻¹ A.

$$* \frac{1}{R_{loop}} = \frac{1}{8.0} + \frac{1}{R}$$

$$\frac{1}{R_{loop}} = \frac{1}{8.0} + \frac{1}{13.3}$$

$$R_{loop} = 5.0 \Omega$$

$$R = \frac{V_R}{I_R} = \frac{10}{0.75} = 13.3 \Omega$$

$$I_R = I_{tot} - I_8 = 2.0 - 1.25 = 0.75 \text{ A}$$


KIRCHHOFF'S RULES

1. Junction rule: The sum of the magnitudes of the currents directed into a junction equals the sum of magnitudes of the currents directed out of the junction.

2. Loop rule: Around any closed-circuit loop, the sum of potential drops equals the sum of potential rises.

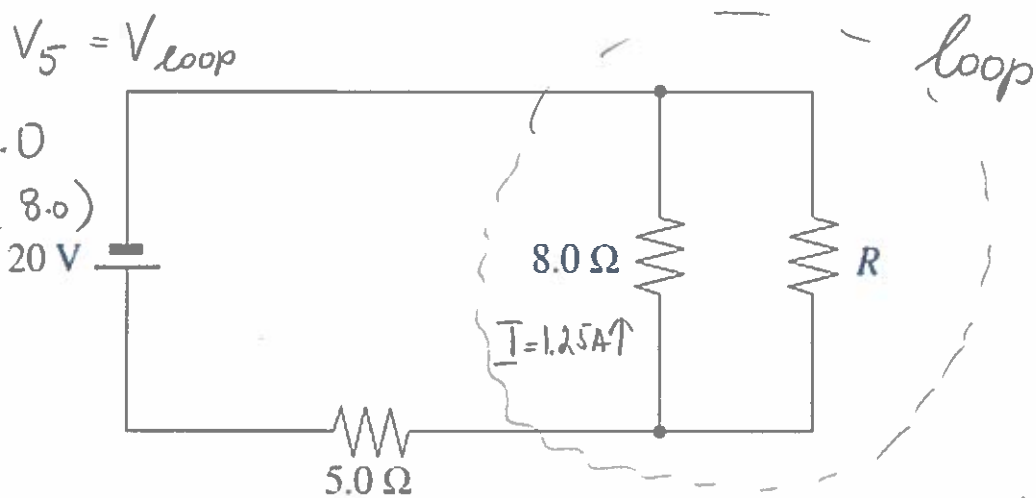Example: Find the equivalent resistance in the circuit given that the current through the 8.0Ω is 1.25 A .

$$\begin{aligned} V_8 &= V_R = V_B - V_5 = V_{loop} \\ &= I_8 \times 8.0 \\ &= (1.25)(8.0) \\ &= \underline{\underline{10 \text{ V}}} \end{aligned}$$



$$V_R = \underline{\underline{10 \text{ V}}}$$

$$\begin{aligned} V_5 &= V_B - V_{loop} \\ &= 20 - 10 \\ &= \underline{\underline{10 \text{ V}}} \end{aligned}$$

$$\begin{aligned} I_{tot} = I_5 &\rightarrow I_5 = \frac{V_B}{R_{eq}} \quad \text{OR} \quad I_{tot} = \frac{V_B - V_{loop}}{5.0} \\ &= \frac{20 - 10}{5.0} \\ &= \underline{\underline{2.0 \text{ A}}} \end{aligned}$$

$$\begin{aligned} R_{eq} &= 5.0 + R_{loop}^* \\ &= 5.0 + 5.0 \\ &= \underline{\underline{10 \Omega}} \end{aligned}$$

$$\text{OR} \quad R_{eq} = \frac{V_B}{I_{tot}} = \frac{20}{2.0} = \underline{\underline{10 \Omega}}$$

$\therefore R_{eq} = 10 \Omega$