


KEY

PHYSICS 11

CIRCUIT ELECTRICITY

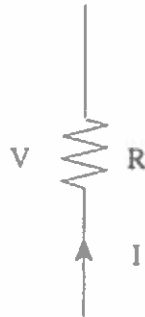1.

Consider the circuit element shown below.



The voltage across the resistor increases from V to $2V$. The resistance remains the same. By what factor has the current changed?

A. $\frac{1}{4}$

B. $\frac{1}{2}$

C. 2

D. 4

$$R_1 = R_2$$
$$V_2 = 2 \cdot V_1$$
$$I_2 = ? \cdot I_1$$

$$I = \frac{V}{R}$$


$$I_1 = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2}{R_2} = \frac{2V_1}{R_1} = 2 \cdot \frac{V_1}{R_1} = 2 \cdot I_1$$

\therefore The current changed by a factor of 2

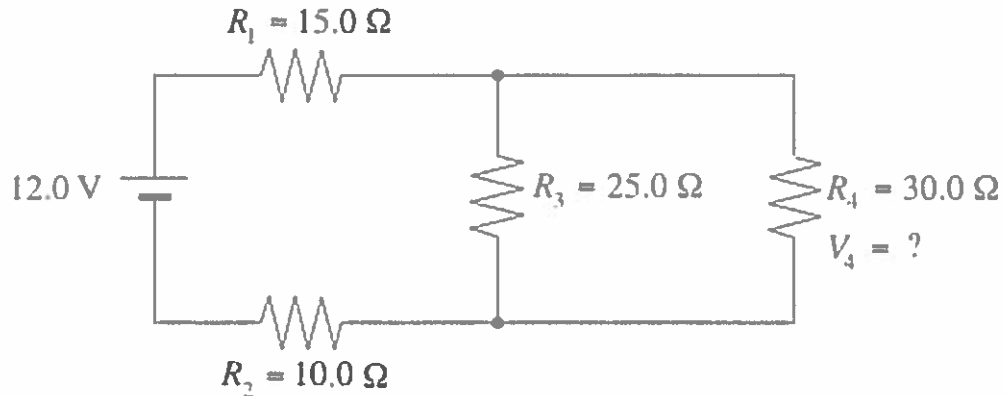2.

A 12.0 V power supply is connected to 4 resistors as shown.



What is the potential difference, V_4 , across the 30.0 Ω resistor?

- A. 2.12 V
- B. 4.24 V**
- C. 9.32 V
- D. 12.0 V

$$V_4 = V_3 = 12 - V_2 - V_1$$

$$\begin{aligned} \bullet \quad R_{eq} &= 15.0 + 10.0 + \frac{1}{\frac{1}{25} + \frac{1}{30}} \\ &= \underline{\underline{38.64 \Omega}} \end{aligned}$$

$$\bullet \quad I_{TOT} = \frac{V_B}{R_{eq}} = \frac{12.0}{38.64} = \underline{\underline{0.31 \text{ A}}}$$

$$\bullet \quad I_{TOT} = I_1 + I_2$$

$$\begin{aligned} \bullet \quad V_1 &= I_1 R_1 \\ &= (0.31)(15) \\ &= \underline{\underline{4.65 \text{ V}}} \end{aligned}$$

$$\begin{aligned} \bullet \quad V_2 &= I_2 R_2 \\ &= (0.31)(10) \\ &= \underline{\underline{3.1 \text{ A}}} \end{aligned}$$

$$\begin{aligned} \bullet \quad V_4 &= 12 - (4.65 + 3.1) \\ &= \underline{\underline{4.25 \text{ V}}} \\ &\quad \uparrow \\ &\quad \text{Some rounding error} \end{aligned}$$

3.

An electric motor is being supplied with 500 W of power at 120 V. The resistance of the motor is 8.0Ω . What current is being supplied to the motor?

- A. 4.2 A
- B. 7.9 A
- C. 15 A
- D. 63 A

$$P = IV$$

$$I = \frac{P}{V}$$

$$= \frac{500}{120}$$

$$= 4.2 \text{ A}$$


4.

A circuit junction is shown below.

$$I_{in} = I_{out}$$

$$0.96 + x = 0.53 + 0.75$$

$$x = 0.32 \text{ A}$$

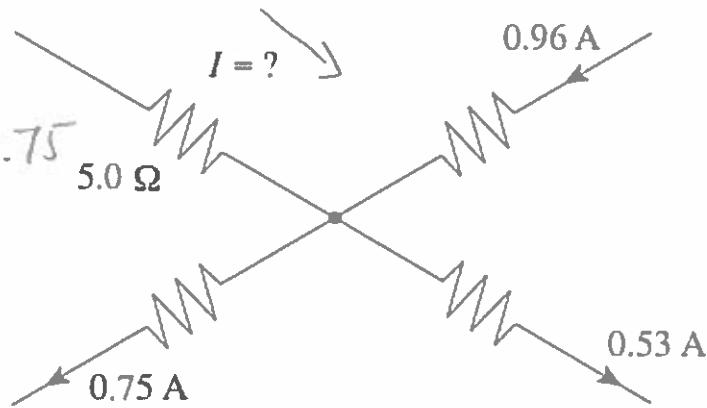

What is the current and its direction through the 5.0Ω resistor?

	CURRENT	DIRECTION
A.	0.32 A ✓	away from junction
<input checked="" type="checkbox"/> B.	0.32 A ✓	towards the junction ✓ *
C.	2.24 A	away from junction
D.	2.24 A	towards the junction

* I must flow into the junction as $0.75 + 0.53 = 1.28 \text{ A}$ flows out and only 0.96 A flows in


5.

A power source is providing a constant voltage, V , to the circuit shown below.

$$R_{eq} = 5 + 7 + \frac{1}{\frac{1}{8} + \frac{1}{10}}$$

$$= 16.4 \Omega$$

$R_{eq} \uparrow$

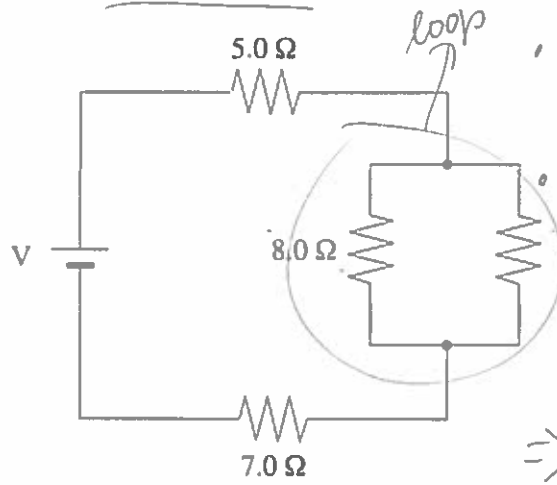

$R = 8 \Omega$ is in parallel with $R = 10 \Omega$

Removing $R = 8 \Omega$ will increase the resistance in the loop.

$$\Rightarrow R_{eq} = 5 + 7 + 10 = 22 \Omega$$

If the 8.0Ω resistor is removed from the circuit what happens to the equivalent resistance of the circuit and the current through the 7.0Ω resistor?

	EQUIVALENT RESISTANCE OF THE CIRCUIT	CURRENT THROUGH 7.0Ω RESISTOR
A.	Increases ✓	Decreases ✓
B.	Decreases	Increases
C.	Increases ✓	Increases
D.	Decreases	Decreases

$$I_{TOT} = I_7$$

$$I = \frac{V_B}{R_{eq}}$$

as $R_{eq} \uparrow$ $I \downarrow$

Note: R and I are inversely proportional, while V and I and V and R are directly proportional.

6.

In an electric circuit, 6.25×10^{18} electrons flow past one point in 0.10 s. What is the current?

- A. 1.6×10^{-19} A
- B. 1.0 A
- C. 10 A
- D. 6.25×10^{19} A

$$I = \frac{q}{\Delta t}$$

$$I = \frac{1.0}{0.10}$$

$$I = 10 \text{ A}$$

$$q = (6.25 \times 10^{18})(1.6 \times 10^{-19})$$

$$q = 1.00 \text{ C}$$


7.

Three identical light bulbs are placed in a circuit as shown.

$R_x = R_y = R_z$

$R_{\text{branch 1}} = R_x + R_y$

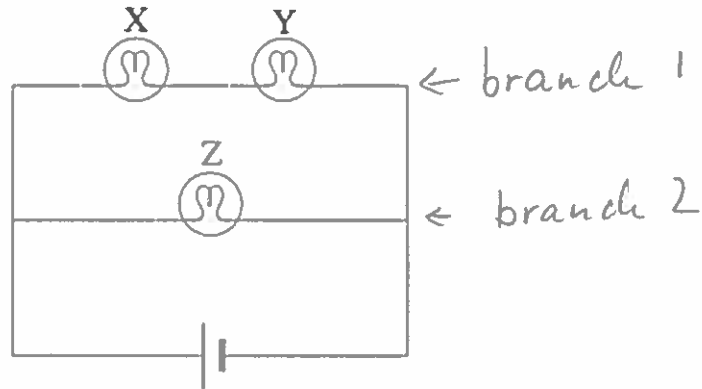$R_{\text{branch 2}} = R_z = \frac{1}{2} R_{\text{branch 1}}$




→ less R more I in branch 2

Which of the following is correct?

- A. The voltage and current are the same for all three bulbs.
- B. The current in light bulb Z is less than the current in light bulb X.
- C. The current in light bulb Z is greater than the current in light bulb Y.**
- D. The voltage across light bulb Z is less than the voltage across light bulb X.

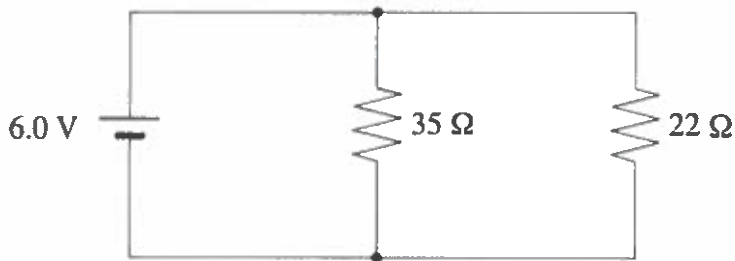8.


What current would be drawn from the power supply in the circuit shown below?



- A. 0.11 A
- B. 0.17 A
- C. 0.27 A
- D. 0.44 A

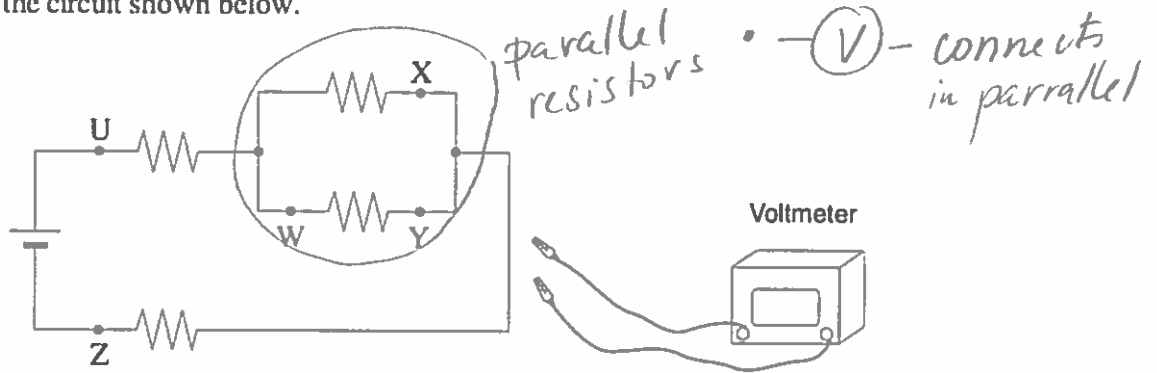
9.

A student needs to connect a voltmeter to measure the potential difference across the parallel resistors in the circuit shown below.




Across which two connection points should the student connect the voltmeter?

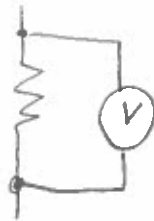- A. U and Z
- B. X and Y
- C. X and W**
- D. W and Z



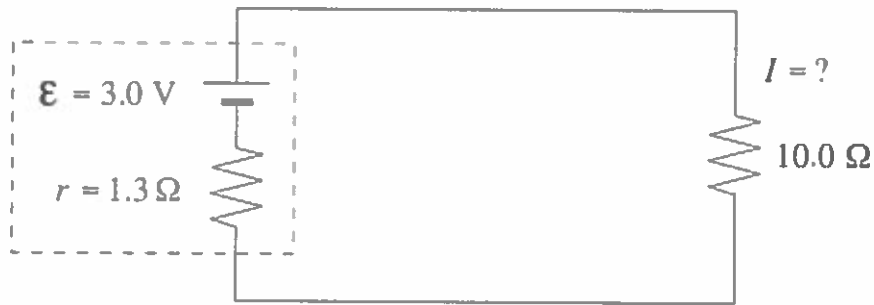10.

What is the current I through the 10.0Ω resistor in the circuit shown below?



- A. 0.27 A**
- B. 0.30 A
- C. 0.34 A
- D. 2.3 A

$$\begin{aligned}
 I_{10} &= I_{tot} = \frac{\mathcal{E}}{R_{eq}} \\
 &= \frac{3.0}{1.3 + 10} \\
 &= \underline{\underline{0.27 \text{ A}}}
 \end{aligned}$$


$$(4) I_{15} = \frac{V_{15}}{R} = \frac{3.0}{15} = \underline{\underline{0.2 A}}$$

11.

What power is dissipated by the 15Ω resistor in the circuit shown?

$$P = VI$$
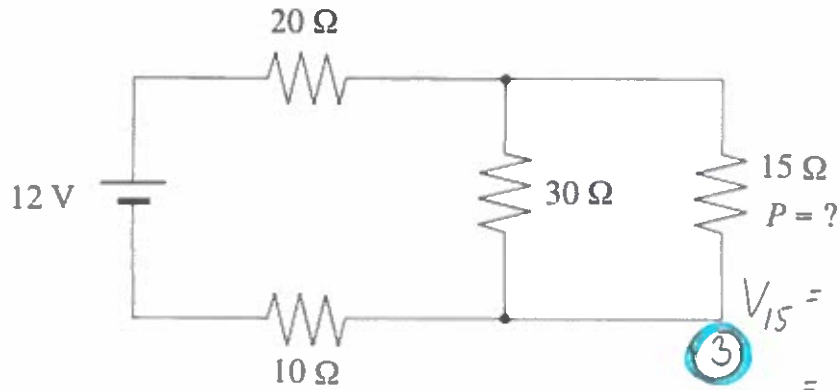
$$(5) P = (3.0)(0.2) = \underline{\underline{0.6 W}}$$



$$V_{15} = V_{loop} = V_B - V_{20} - V_{10} = 12 - (20)(0.3) - (10)(0.3) = \underline{\underline{3.0 V}}$$

- A. 0.60 W
- B. 1.4 W
- C. 6.7 W
- D. 15 W


$$I_{15} = ?$$

$$(2) I_{TOT} = \frac{V_B}{R_{eq}} = \frac{12}{40} = \underline{\underline{0.30 A}}$$

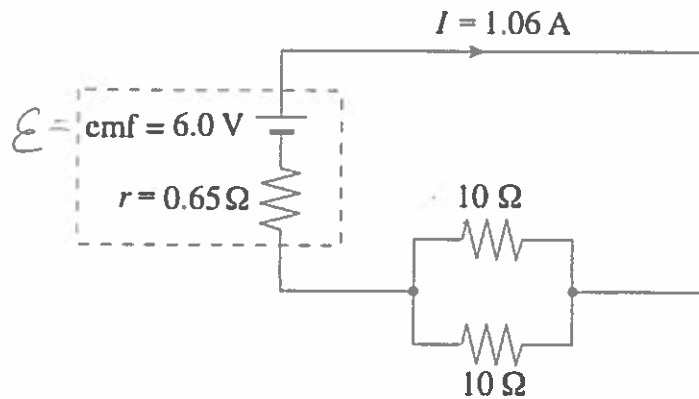12.

$$(1) R_{eq} = 20 + 10 + \frac{1}{\frac{1}{30} + \frac{1}{15}} = \underline{\underline{40 \Omega}}$$

What is the terminal voltage of the battery in the circuit shown?



$$V_{term} = \mathcal{E} - Ir = 6.0 - (1.06)(0.65) = \underline{\underline{5.311 V}}$$

- A. 0.69 V
- B. 5.3 V
- C. 6.0 V
- D. 6.7 V