

FINDING INFORMATION ABOUT MORE COMPLEX CIRCUITS


Parallel:

$$\frac{1}{\Sigma R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Series:

$$\Sigma R = R_1 + R_2 + \dots + R_n$$

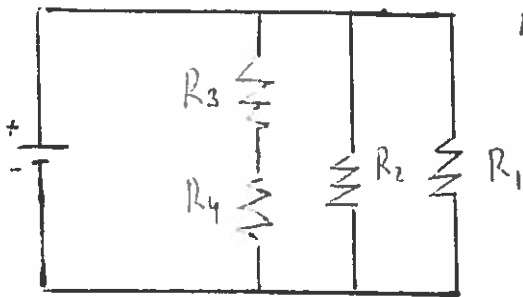1. Find the equivalent resistance of the electric circuit below:



$$R_1 = 10\Omega, R_2 = 5\Omega, R_3 = 8\Omega, R_4 = 4\Omega$$


$$R_3 + R_4 = 12\Omega$$

$$\Sigma R: \frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{5} + \frac{1}{12} = \frac{6+12+5}{60} = \frac{23}{60}$$

$$\therefore \Sigma R = \frac{60}{23}\Omega = 2.6\Omega$$

- Before using the formula for equivalent resistance for resistors in parallel R_3 and R_4 must be added using the formula for resistors in series.

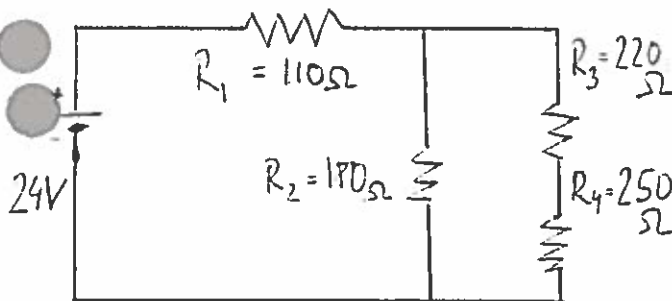2. Find the current in the electric circuit below:



$$R_3 + R_4 = 220 + 250 = 470\Omega$$

$$R_p: \frac{1}{\Sigma R_p} = \frac{1}{180} + \frac{1}{470} = \frac{470 + 180}{84600} = \frac{650}{84600} \Rightarrow \Sigma R_p = \frac{84600}{650} = 130\Omega$$

$$\Sigma R: R_1 + 130\Omega = 110 + 130 = 240\Omega$$

$$I = \frac{V}{R} = \frac{24}{240} = \underline{\underline{0.1\text{ A}}}$$

Step 1: locate all resistors in parallel R_2 , R_4 , and R_3 Step 2: add R_3 and R_4 using the formula for resistors in seriesStep 3: Find the resistance from R_2 and $(R_3 + R_4)$ using the formula for resistors in parallelStep 4: Find the equivalent resistance using the result from step 3 and adding R_1 using the formula for resistors in series


Step 5: Use Ohm's law to find the electric current

Potential rise : from - to + 6V across the battery

Potential drop : from + to - $V_{loop} + V_3 + V_4 \Rightarrow \bar{V}_{loop} = \Sigma \text{rise} - \Sigma \text{drop}$

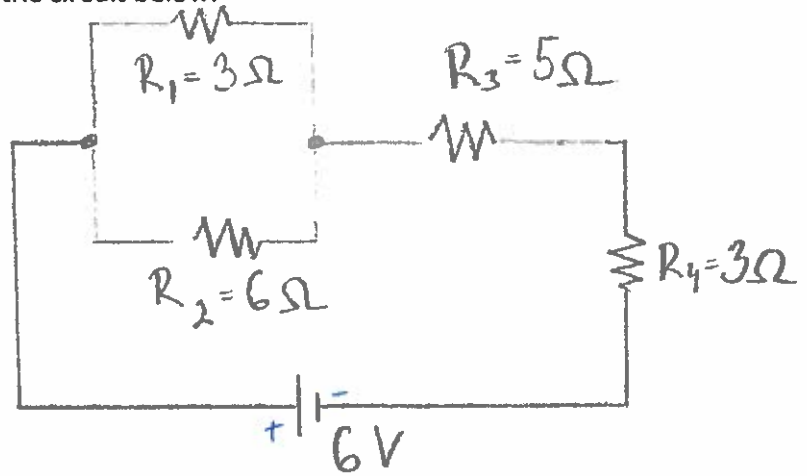3. Find as much information as you can about the electric circuit below:

- Find the equivalent resistance
- Find the electric current at the battery
- Find the electric current for each resistor
- Find the potential in every closed loop using the Second Kirchhoff's Rule
($\Sigma V_{\text{battery}} = \Sigma V_{\text{resistors in a loop}}$)
- Use Ohm's Law to find missing information when 2 out of 3 quantities are known



$$\Sigma R = R_4 + R_3 + R_p$$
$$= 3 + 5 + 2 = \underline{\underline{10\Omega}}$$

$$\frac{1}{R_p} = \frac{1}{6} + \frac{1}{3}$$
$$= \frac{1+2}{6} = \frac{3}{6}$$
$$R_p = \frac{6}{3} = 2\Omega$$

$$I_{\text{bat.}} = \frac{V_{\text{bat.}}}{R_{\text{eq}}} = \frac{6}{10} = \underline{\underline{0.6\text{ A}}}$$

$$I_4 = I_3 = I_{\text{battery}} = 0.6\text{ A}$$

⚠ to find I_1 and I_2 V_1 and V_2 must be known first

$$\text{but } V_{\text{battery}} = V_4 + V_3 + V_{\text{loop}}$$

$$V_4 = (3)(0.6) = \underline{1.8\text{ V}}$$
$$V_3 = (5)(0.6) = \underline{\underline{3.0\text{ V}}}$$

$$6 = 1.8 + 3.0 + V_{\text{loop}}$$
$$\therefore V_{\text{loop}} = 6 - 3.0 - 1.8$$
$$= \underline{\underline{1.2\text{ V}}}$$

Recall: Resistors in parallel have the same voltage across each R

$$\therefore V_1 = V_2 = V_{\text{loop}} = 1.2\text{ V}$$

$$I_1 = \frac{V_1}{R_1} = \frac{1.2}{3} = \underline{\underline{0.4\text{ A}}}$$

$$I_2 = \frac{V_2}{R_2} = \frac{1.2}{6} = \underline{\underline{0.2\text{ A}}}$$