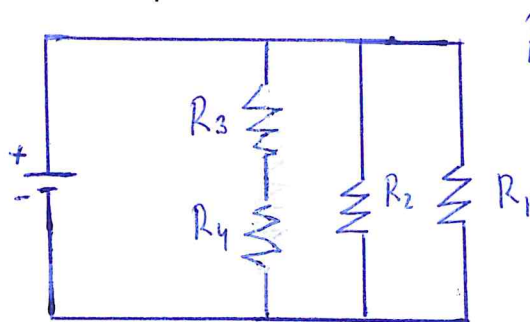


FINDING INFORMATION ABOUT MORE COMPLEX CIRCUITS

Parallel:

Series:


1. Find the equivalent resistance of the electric circuit below:



$$R_1 = 10\Omega, R_2 = 5\Omega, R_3 = 8\Omega, R_4 = 4\Omega$$

- Before using the formula for equivalent resistance for resistors in parallel R_3 and R_2 must be added using the formula for resistors in series.

2. Find the current in the electric circuit below:

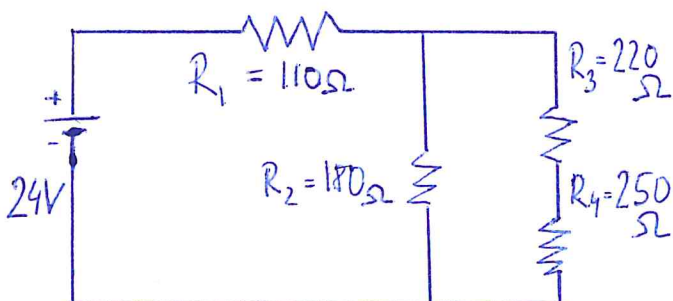**Step 1:** locate all resistors in parallel _____, _____, and _____**Step 2:** add R_3 and R_4 using the formula for resistors in series**Step 3:** Find the resistance from R_2 and $(R_3 + R_4)$ using the formula for resistors in parallel**Step 4:** Find the equivalent resistance using the result from step 3 and adding R_1 using the formula for resistors in series**Step 5:** Use Ohm's law to find the electric current

3. Find as much information as you can about the electric circuit below:

- Find the equivalent resistance
- Find the electric current at the battery
- Find the electric current for each resistor
- Find the potential in every closed loop using the Second Kirchhoff's Rule
($\sum V_{\text{battery}} = \sum V_{\text{resistors in a loop}}$)
- Use Ohm's Law to find missing information when 2 out of 3 quantities are known

