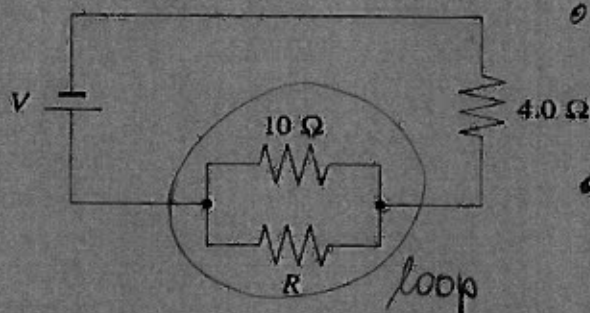


1.

What value of R in the circuit shown below will cause the parallel combination ($10\ \Omega$ and R) to dissipate the same power as the $4.0\ \Omega$ resistor?



$$P = IV = I^2R$$

$$P_{\text{loop}} = P_4 \Leftrightarrow R_{\text{loop}} = 4.0\ \Omega$$

$$4 = \frac{10R}{R+10}$$

$$4(R+10) = 10R$$

$$4R + 40 = 10R$$


$$\frac{40}{6} = \frac{6R}{6}$$

$$R = 6.7\ \Omega$$

- A. $0.26\ \Omega$
 B. $2.9\ \Omega$
 C. $6.0\ \Omega$
 D. $6.7\ \Omega$

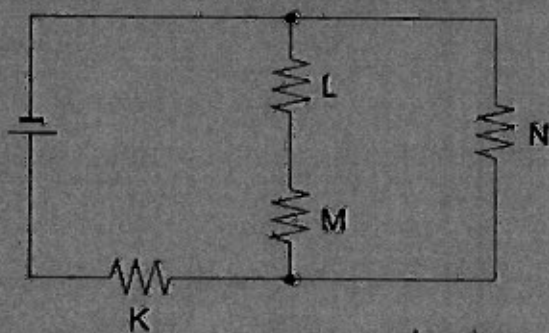2.

All the resistors shown in the circuit have the same resistance value.



$$R_L = R_N = R_M = R_K$$

Which resistor dissipates the most heat?

- A. K
 B. L
 C. M
 D. N

Find the greatest P as $P = \frac{Q}{\Delta t}$

$$P = IV = I^2R$$

\Rightarrow if R is the same for all then the greatest P is caused by the greatest current (I)

$= P_K$ has the largest I : $I_K = I_{\text{TOT}}$

3.

before


1. A resistor is added in parallel to the 4.0Ω resistor shown in the diagram below.

After:

$$R_{eq} = 4 + \frac{1}{\frac{1}{8} + \frac{1}{10}}$$

$$= 4 + 4.7$$

$$= 8.7 \Omega$$

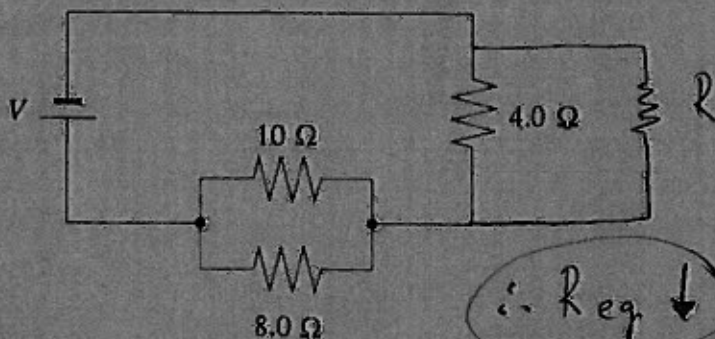

$$R_{eq} = \frac{1}{\frac{1}{10} + \frac{1}{8}} + \frac{1}{\frac{1}{4} + \frac{1}{R}}$$

$$= 4.7 + \frac{1}{\frac{R+4}{4R}}$$

$$= 4.7 + \frac{4R}{R+4}$$

$\therefore R_{eq} \downarrow$

$$\frac{4R}{4R} < 4$$

as $4R < 4(4+R)$
 $4R < 16 + 4R$ ✓

What happens to the power dissipated by the 8.0Ω resistor and by the 4.0Ω resistor?

	$P_{8.0 \Omega}$	$P_{4.0 \Omega}$
A.	decreases	increases
B.	decreases	decreases ✓
C.	increases ✓	increases
D.	increases ✓	decreases ✓

Observations:

$$R_{eq} \downarrow$$

$$I_4 \downarrow \Rightarrow P_4 \downarrow$$

$$P = IV = I^2 R$$

V is constant,
 if $R_{eq} \downarrow$


$$\text{as } I_{TOT} = \frac{V_B}{R_{eq}} \text{ then } I_{TOT} \uparrow$$

$$\text{if } I_{TOT} \uparrow, \text{ then } I_8 \uparrow$$

$$\text{thus } P_8 \uparrow$$

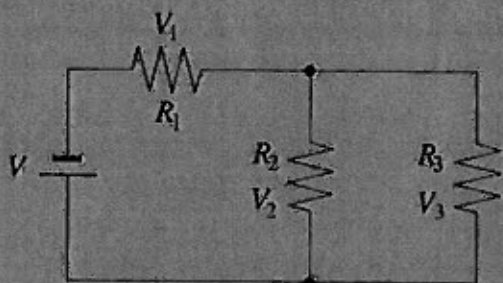4.

Which of the following statements is true for the electric circuit shown below, regardless of the resistors used?




$$\bullet V_2 = V_3 \quad (\text{parallel } R)$$

$$\bullet V = V_1 + V_2 = V_1 + V_3$$

- A. $V_1 = V_2$
 B. $V = V_2 + V_3$
 C. $V = V_1 + V_3$ ✓
 D. $V = V_1 + V_2 + V_3$

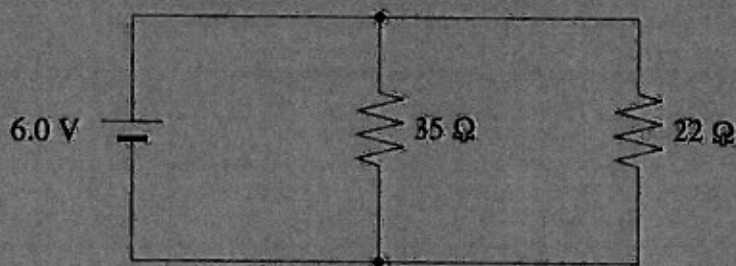5.

What current would be drawn from the power supply in the circuit shown below?



- A. 0.11 A
 B. 0.17 A
 C. 0.27 A
 D. 0.44 A

$$I_{TOT} = \frac{V_B}{R_{eq}} = \frac{6.0}{13.5\dots} = \underline{\underline{0.44 \text{ A}}}$$

$$R_{eq} : \frac{1}{R_{loop}} = \frac{1}{\frac{1}{35} + \frac{1}{22}} = 13.508\dots \Omega$$