

KEY


## ELECTRIC CIRCUITS 2

1.


Which arrangement of four identical resistors has the highest equivalent resistance?

Let  $R = 2\ \Omega$


A.

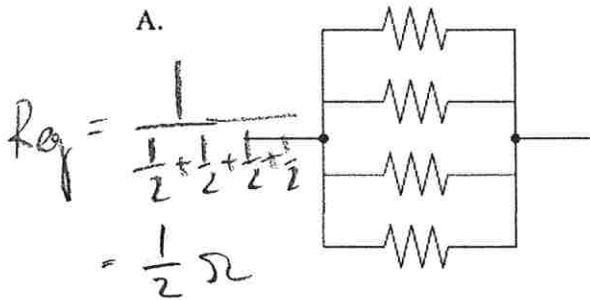


B.

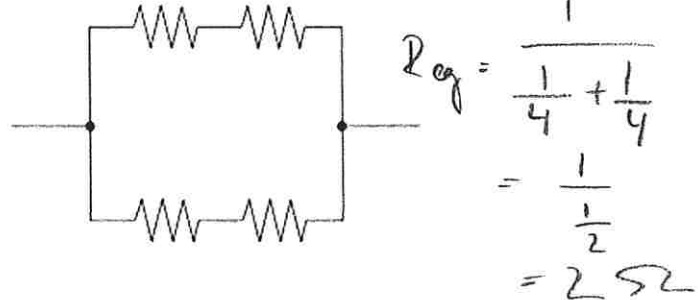

C.

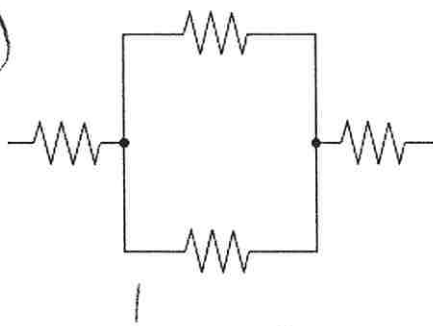

D.

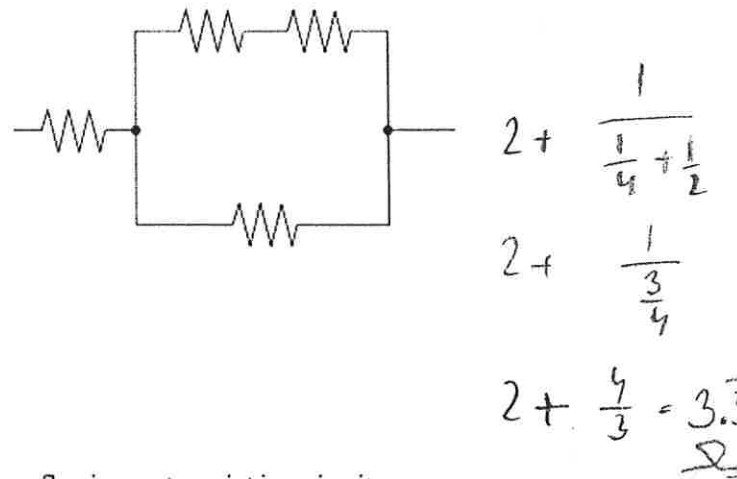

2.  $2 + \frac{1}{\frac{1}{2} + \frac{1}{2}} + 2 = 2 + 1 = 5\ \Omega$

A student is instructed to determine the amount of charge flowing past a point in a circuit of unknown resistance during an experiment. What equipment will permit the student to do this?


- A. voltmeter
- B. ammeter, voltmeter
- C. ammeter, stopwatch
- D. voltmeter, stopwatch

$I = \frac{q}{\Delta t}$  ← stopwatch  
↑  
ammeter

$\rightarrow q = I \cdot \Delta t$

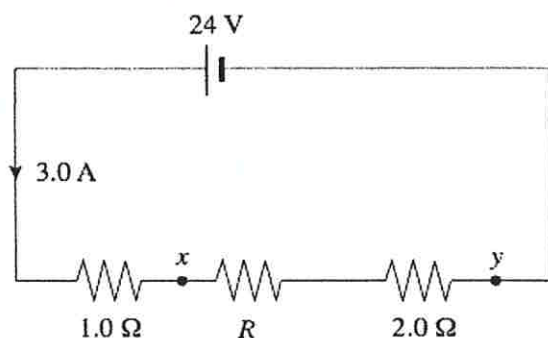3.

A series circuit consists of a battery and three resistors arranged as shown in the diagram below.



$$R_{eq} = \frac{24}{3.0} = 8.0 \Omega$$

$$R = 8.0 - 1.0 - 2.0 = 5.0 \Omega$$


$$V_{xy} = (R_{x+y})(I_{TOT}) = (7.0)(3.0) = 21 V$$

What is the potential difference  $V_{xy}$ ?

- A. 3.0 V
- B. 6.0 V
- C. 9.0 V
- ☒ D. 21 V

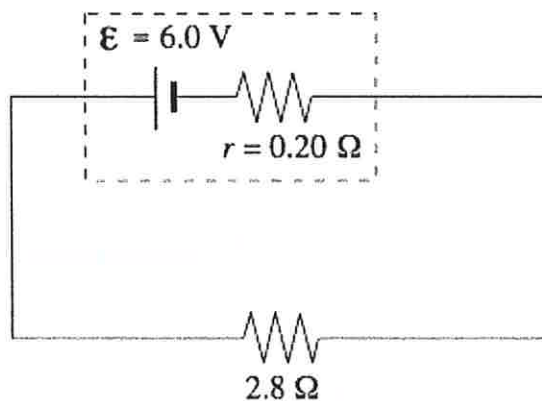4.

What is the battery's terminal voltage in the circuit below?



$$I_{TOT} = \frac{\mathcal{E}}{R_{eq}} = \frac{6.0}{(2.8 + 0.20)} = \frac{6.0}{3.0} = 2.0 A$$

- A. 0.40 V
- ☒ B. 5.6 V
- C. 6.0 V
- D. 6.4 V

$$V_{term} = \mathcal{E} - I r = 6.0 - (2.0)(0.20) = 6.0 - 0.4 = \boxed{5.6 V}$$