

ELECTRIC CIRCUITS 3


1.

Which of the following statements provides valid reasoning for the transmission of electric energy at high potential?

- A. At high potential there will be low current resulting in low power loss.
- B. At high potential there will be high current resulting in high power loss.
- C. At high potential there will be low line resistance resulting in low power loss.
- D. At high potential there will be high line resistance resulting in high power loss.

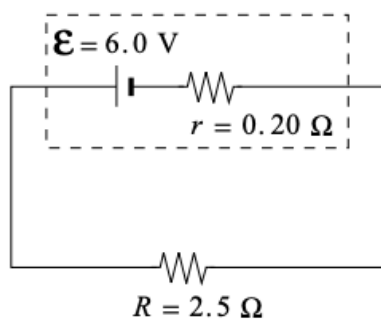2.


What is the terminal voltage of the battery in the circuit shown in the diagram?



- A. 0.44 V
- B. 5.6 V
- C. 6.0 V
- D. 6.4 V

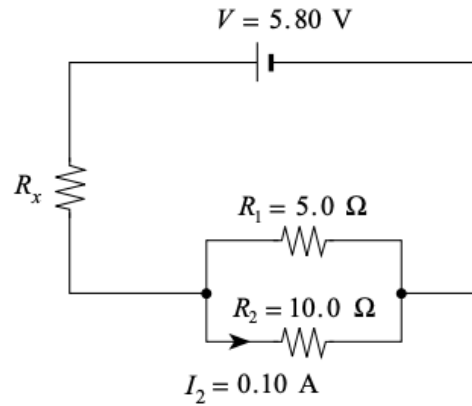3.





What is the power dissipated in the unknown resistor R_x in the circuit below?



- A. 0.30 W
- B. 1.4 W
- C. 1.7 W
- D. 2.0 W

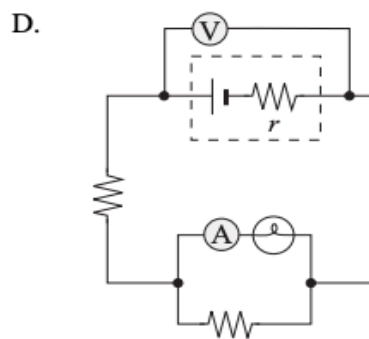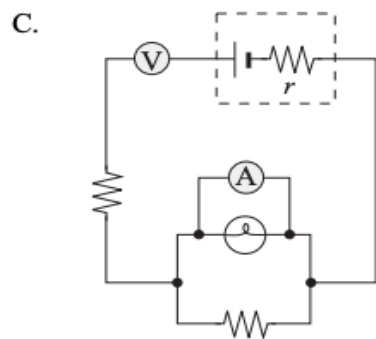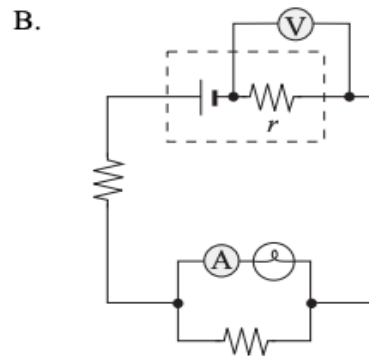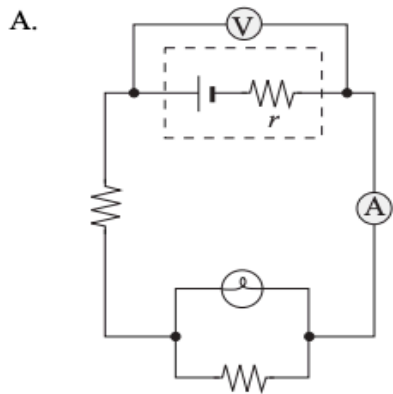
4.

In which of the following circuits is the voltmeter placed correctly to measure the terminal voltage of the battery, and the ammeter placed correctly to measure the current through the light bulb (\odot) ?



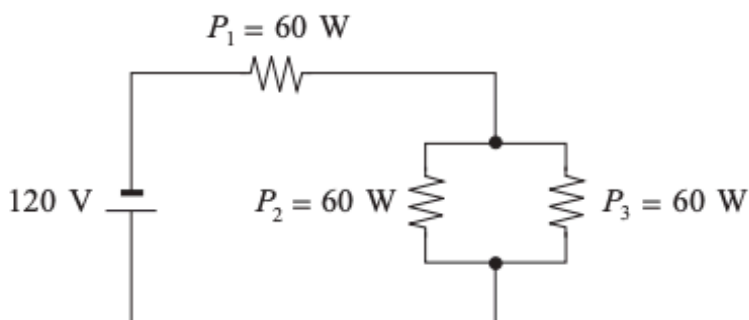5.


What is the current leaving the battery in the circuit below?



- A. 1.3 A
- B. 1.5 A
- C. 2.0 A
- D. 4.0 A

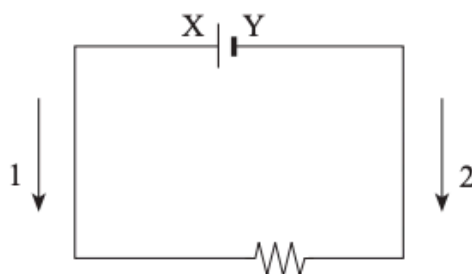6.


Which of the following correctly labels arrows 1 and 2 and polarities X and Y in the circuit below?



	ARROW 1	ARROW 2	POLARITY X	POLARITY Y
A.	Electron Flow	Conventional Current	Positive	Negative
B.	Electron Flow	Conventional Current	Negative	Positive
C.	Conventional Current	Electron Flow	Positive	Negative
D.	Conventional Current	Electron Flow	Negative	Positive

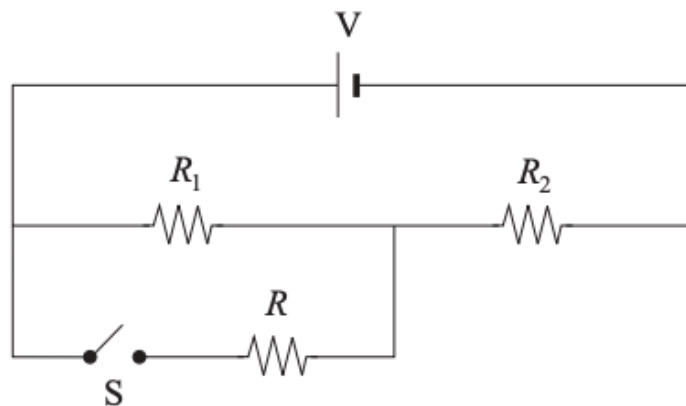7.

Switch S is originally open as shown in the circuit below.




How does the current through resistors R_1 and R_2 change when switch S is closed?

	CURRENT THROUGH R_1	CURRENT THROUGH R_2
A.	increases	increases
B.	increases	decreases
C.	decreases	increases
D.	decreases	decreases

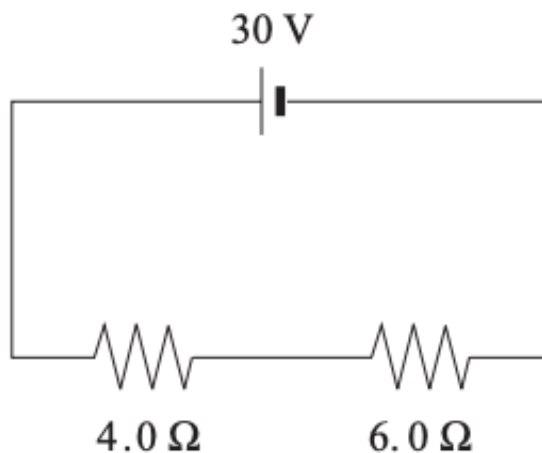8.

What is the power output of the 6.0Ω resistor in the diagram?



- A. 36 W
- B. 54 W
- C. 90 W
- D. 150 W


9.

A 12 V power supply is connected to an 8.0Ω resistor for 50 s. How much charge passes through the resistor?

- A. 1.9 C
- B. 75 C
- C. 900 C
- D. 4 800 C

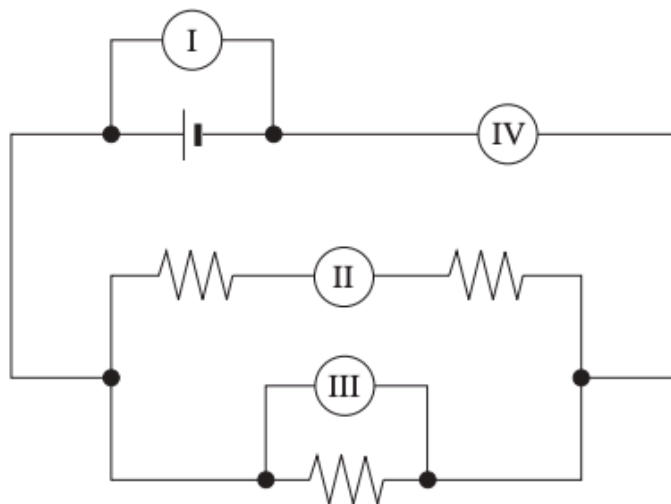10.

The circuit shown below includes two ammeters and two voltmeters. Identify the correct placement of these meters.



	AMMETERS	VOLTMETERS
A.	I, II	III, IV
B.	I, III	II, IV
C.	II, IV	I, III
D.	III, IV	I, II


11.

A 120 V supply is connected to a heater of resistance $15\ \Omega$. What must the resistance of another heater be in order to produce the same power output when connected to a 240 V supply?

- A. $3.8\ \Omega$
- B. $7.5\ \Omega$
- C. $30\ \Omega$
- D. $60\ \Omega$

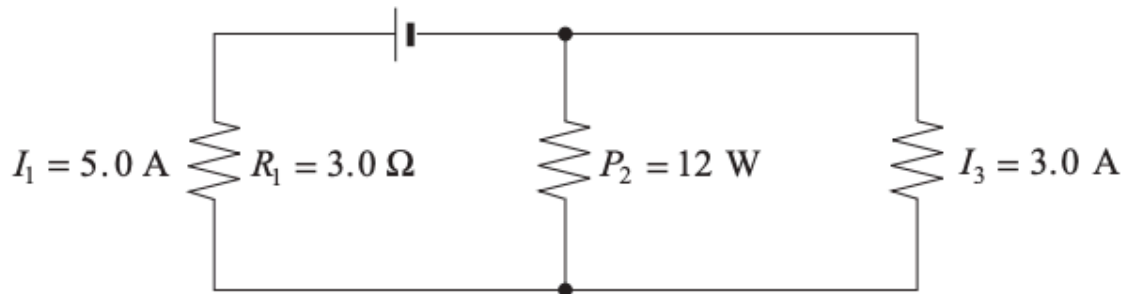12.

What is the voltage of the power supply shown in the diagram?



- A. 12 V
- B. 19 V
- C. 21 V
- D. 27 V