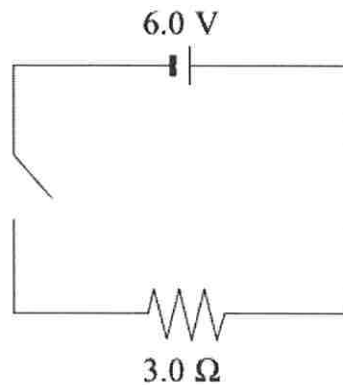


ELECTRIC CIRCUITS 4

1.

A 6.0 V battery is connected through a switch to a $3.0\ \Omega$ resistor as shown below.







What total charge flows through the resistor if the switch is closed for 40 s ?

- A. $2.0 \times 10^{-9}\text{ C}$
- B. 2.0 C
- C. 80 C
- D. 480 C

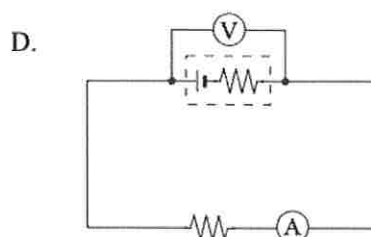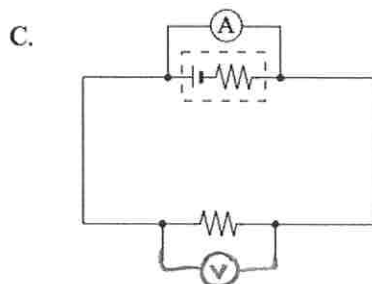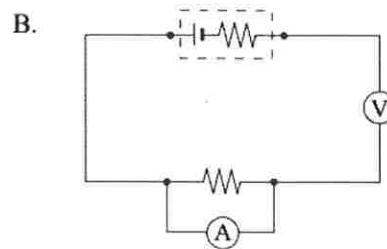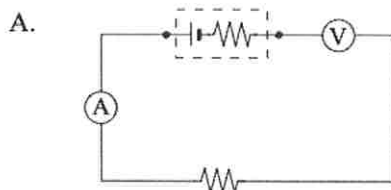
2.

Which of the following diagrams shows meters correctly placed to measure the circuit current and the terminal voltage of the battery?



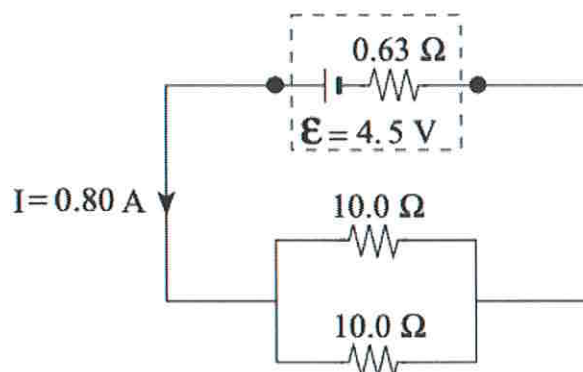3.


. What is the terminal voltage of the cell in the circuit shown in the diagram below?



- A. 0.50 V
- B. 3.5 V
- C. 4.0 V
- D. 4.5 V

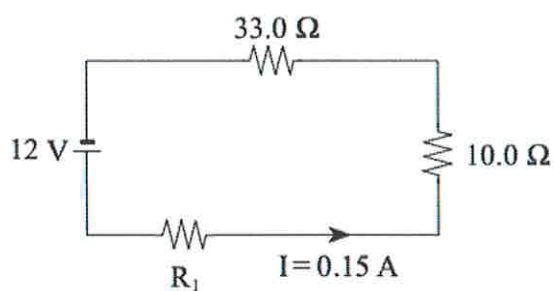4.


What is the power dissipated in resistor R_1 in the circuit shown in the diagram below?



- A. 0.83 W
- B. 0.97 W
- C. 1.8 W
- D. 2.8 W

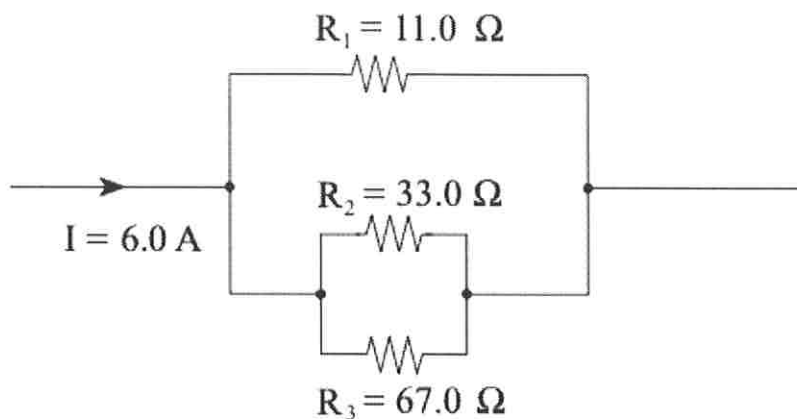5.

The diagram below shows part of an electrical circuit.




What is the current through resistor R_1 ?

- A. 2.0 A
- B. 3.0 A
- C. 4.0 A
- D. 6.0 A

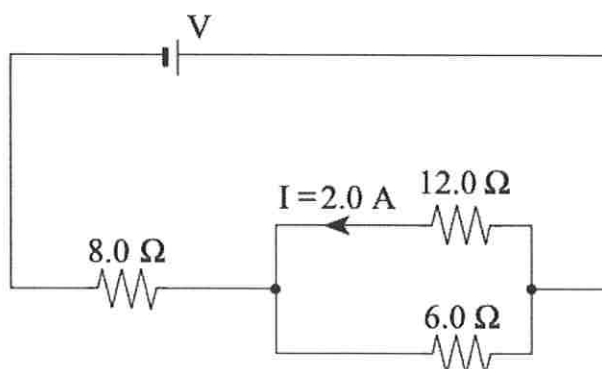6.


What is the voltage, V , of the power supply shown in the circuit?



- A. 24 V
- B. 52 V
- C. 72 V
- D. 96 V

7.


What is the emf of the battery shown?

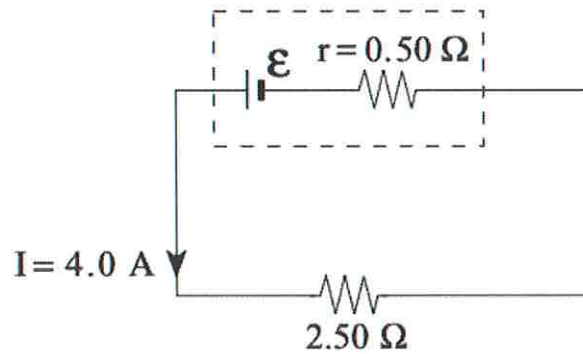

- A. 2.0 V
- B. 8.0 V
- C. 10 V
- D. 12 V

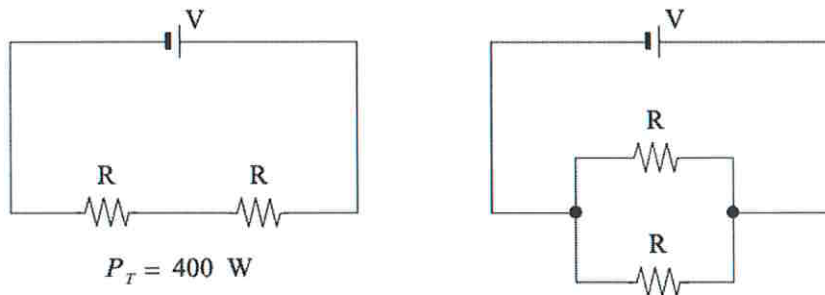8.





Two identical resistors connected in series have a **total** power output of 400 W. Assuming V and R remain constant, what would the total power output be when the resistors are re-connected in parallel?



- A. 200 W
- B. 400 W
- C. 800 W
- D. 1 600 W


9.

Which of the following correctly shows the direction of conventional current and electron flow?

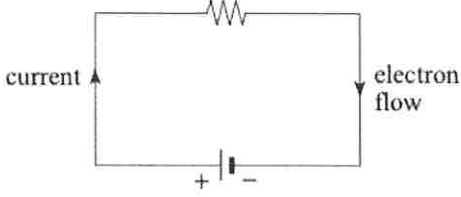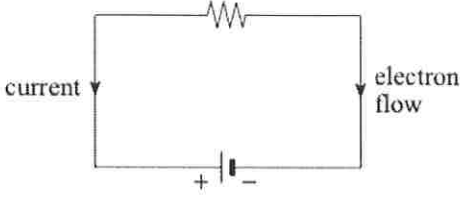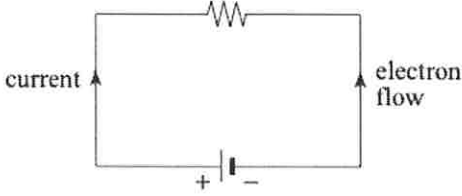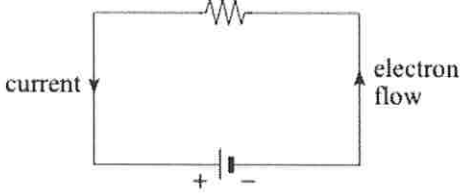- A. 
- B. 
- C. 
- D. 

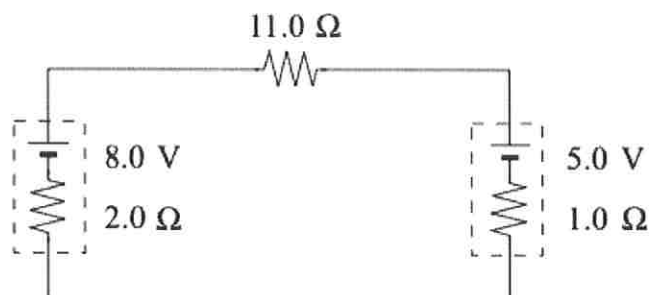10.


What current flows through the $11.0\ \Omega$ resistor?



- A. 0.21 A
 B. 0.27 A
 C. 0.93 A
 D. 1.2 A

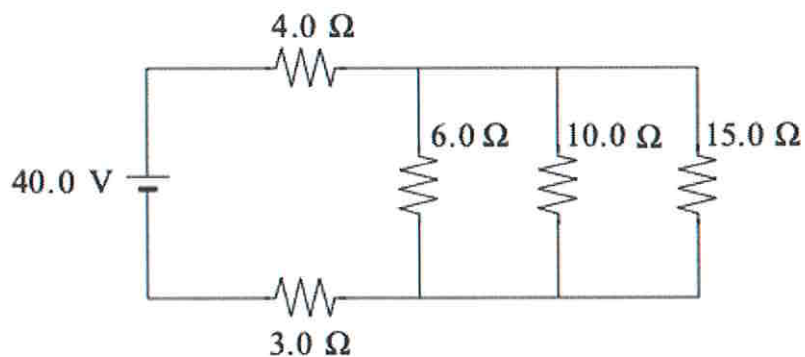11.


Calculate the current through the $6.0\ \Omega$ resistor in the circuit shown.



- A. 1.1 A
- B. 2.0 A
- C. 4.0 A
- D. 6.7 A

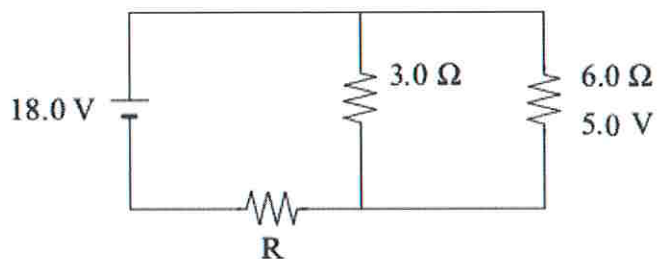12.

In the following circuit, determine the value of resistor R.



- A. $3.2\ \Omega$
- B. $5.2\ \Omega$
- C. $9.0\ \Omega$
- D. $23\ \Omega$

13.

A battery provides 3.20 W of power to an external resistance. What power is dissipated as heat by the internal resistance within the battery?



- A. 0.19 W
- B. 3.4 W
- C. 3.6 W
- D. 60 W

14.

A 75 W bulb is connected across a 120 V source. While the bulb is lighted, what is the effective resistance of the bulb?

- A. 0.62 Ω
- B. 1.6 Ω
- C. 47 Ω
- D. 190 Ω

