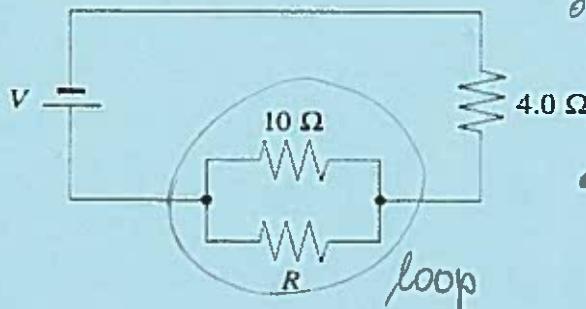


KEY

ELECTRIC CIRCUITS

1.


What value of R in the circuit shown below will cause the parallel combination ($10\ \Omega$ and R) to dissipate the same power as the $4.0\ \Omega$ resistor?



- A. $0.26\ \Omega$
- B. $2.9\ \Omega$
- C. $6.0\ \Omega$
- D.** $6.7\ \Omega$

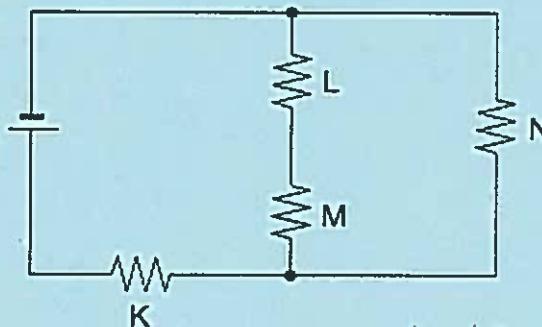2.

All the resistors shown in the circuit have the same resistance value.



Which resistor dissipates the most heat?

- A.** K
- B. L
- C. M
- D. N

$$\bullet P = IV = I^2R$$

$$\bullet P_{loop} = P_4 \Leftrightarrow R_{loop} = 4.0\ \Omega$$

$$4 = \frac{10R}{(R+10)}$$

$$4(R+10) = 10R$$

$$4R + 40 = 10R$$

$$\frac{40}{6} = \frac{6R}{6}$$

$$R = 6.7\ \Omega$$

$$\bullet R_L = R_N = R_M = R_K$$

Find the greatest P as $P = \frac{Q}{t}$

$$P = IV = I^2R$$

\Rightarrow if R is the same for all

then the greatest P is caused by the greatest current (I)


$= R_L$ has the largest I : $I_L = I_{TOT}$

3.

before

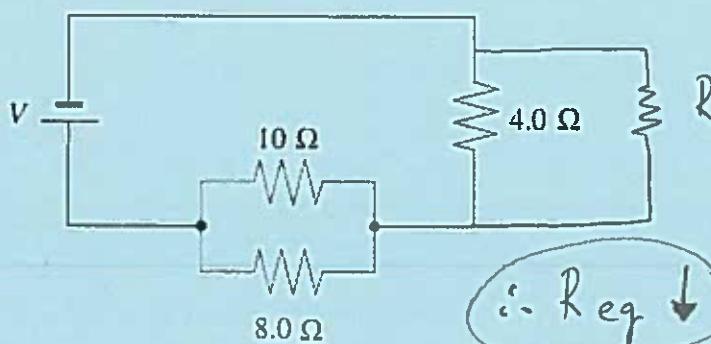- i. A resistor is added in parallel to the $4.0\ \Omega$ resistor shown in the diagram below.

$$\begin{aligned} R_{eq} &= 4 + \frac{1}{\frac{1}{8} + \frac{1}{10}} \\ &= 4 + 4.4 \\ &= 8.4\ \Omega \end{aligned}$$



after:

$$\begin{aligned} R_{eq} &= \frac{1}{\frac{1}{10} + \frac{1}{8}} + \frac{1}{\frac{1}{4} + \frac{1}{R}} \\ &= 4.4 + \frac{1}{R+4} \\ &= 4.4 + \frac{4R}{R+4} \end{aligned}$$

$\therefore R_{eq} \downarrow$

$$\frac{4R}{4+R} < 4$$

$$4R < 4(4+R)$$

$$4R < 16 + 4R$$

What happens to the power dissipated by the $8.0\ \Omega$ resistor and by the $4.0\ \Omega$ resistor?

	$P_{8.0\Omega}$	$P_{4.0\Omega}$
A.	decreases	increases
B.	decreases	decreases
C.	increases	increases
D.	increases	decreases

Observations:

$$R_{eq} \downarrow$$

$$I_4 \downarrow \Rightarrow P_4 \downarrow$$

$$P = IV = I^2 R$$

V is constant,
if $R_{eq} \downarrow$


$$\text{as } I_{TOT} = \frac{V_B}{R_{eq}} \text{ then } I_{TOT} \uparrow$$

if $I_{TOT} \uparrow$, then $I_8 \uparrow$

$$\text{thus } P_8 \uparrow$$

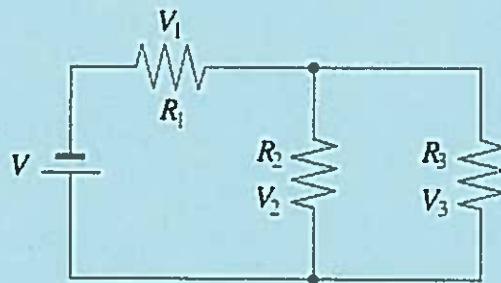4.

Which of the following statements is true for the electric circuit shown below, regardless of the resistors used?




$$\bullet V_2 = V_3 \text{ (parallel R)}$$

$$\bullet V = V_1 + V_2 = V_1 + V_3$$

- A. $V_1 = V_2$
- B. $V = V_2 + V_3$
- C. $V = V_1 + V_3$
- D. $V = V_1 + V_2 + V_3$

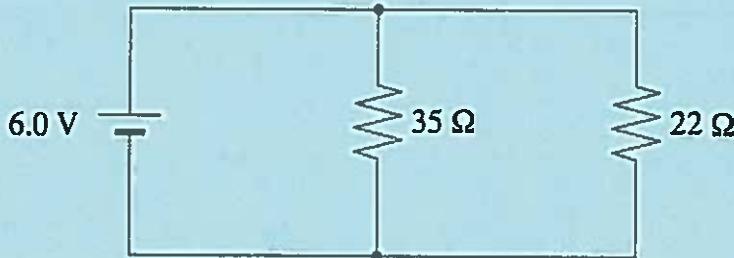5.

What current would be drawn from the power supply in the circuit shown below?



- A. 0.11 A
- B. 0.17 A
- C. 0.27 A
- D. 0.44 A

$$I_{TOT} = \frac{V_B}{R_{eq}} = \frac{6.0}{13.5\ldots} \therefore \underline{\underline{0.44 A}}$$

$$R_{eq}: \frac{1}{R_{loop}} = \frac{1}{\frac{1}{35} + \frac{1}{22}} = 13.508\ldots \Omega$$

