

Electric Circuits – components and symbols

Wire	
Switch	
Resistor	
Cell	
Battery	
Light Bulb	
Ammeter	
Voltmeter	

Direction of Electric Current

Conventional

True

POWER

