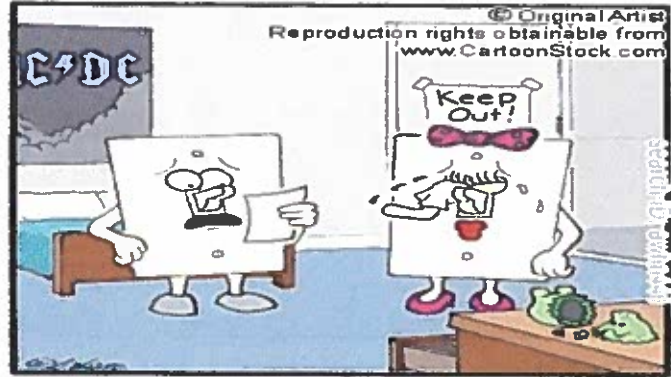


## PHYSICS

## ELECTRIC CIRCUITS AND OHM'S LAW



1. If a battery delivers a current of  $0.68\text{mA}$ , how much charge passes through a circuit powered by this battery in 1 hour?
2. How much time is needed for  $500\mu\text{C}$  of charge to pass through a current of  $0.2\text{mA}$ ?
3.  $10^{10}$  electrons pass through a wire in 1 minute. What is the current?
4. How many electrons per second pass through a wire carrying current of  $20\text{A}$ ?

## Resistance

**Resistance** is the ratio of the voltage applied to a material to the current that passes through the material.

**High Resistance** = only a small portion of charge is able to pass through the material

**Low Resistance** = most of the charge passes through the material

Symbol: \_\_\_\_\_ Units: \_\_\_\_\_

**Resistor** = material or a device that resist the flow of charges

- Reduces the electric current
- Symbol in an electric circuit:

**Resistivity** = property unique to every material. Same material will have same resistivity.

**Resistance** = given by resistivity and by the size and shape of the material.

Small resistance:

Large resistance:

**Equivalent Resistance = Net Resistance =  $\sum R = R_{eq}$**

## Ohm's Law

## Resistors in Series

- If one resistor is disconnected the flow of the current stops to flow to all the other resistors
- Total voltage is equal to the sum of the voltages across each resistor
- Same current flows through each resistor
- **Ammeter must be connected in series**

$$R_{eq} = R_1 + R_2 + \dots + R_n$$

## Resistors in Parallel

- The current from a source splits into separate paths
- When one resistor is disconnected the current still flows through the rest of the resistors
- Same voltage is applied across each resistor
- **Voltmeter must be connected in parallel**

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

1. A current  $I$  entering A has three possible paths.  
Hence it divides into  $I_1$ ,  $I_2$ , and  $I_3$ .

2. Points such as A, B, C, and D are called

\_\_\_\_\_ or \_\_\_\_\_.

3. A round trip such as

$A \rightarrow B \rightarrow C \rightarrow A$  or  $A \rightarrow B \rightarrow C \rightarrow D \rightarrow A$

are called \_\_\_\_\_.

## Kirchhoff's Rules

1. At any node, sum of incoming current equal the sum of outgoing current.
2. Sum of potential differences (or voltage) across all elements in a loop is zero.

## **MURPHY'S LAW**

**What can go wrong, will go wrong.**

Essentially, the laws of nature always work, whether we are paying attention or not.

**(Equipment blows to protect fuses.)**

**(Interchangeable parts aren't & fail-safes don't.)**

**Mrs MURPHY'S COROLLARY**

**Murphy is too much of an optimist.**