

PRACTICE TEST

Name: _____

1. Three charges of identical magnitude are arranged as shown.

$Q_1 \oplus$

$Q_2 \oplus$

$\ominus Q_3$

What is the direction of the electric force on Q_2 ?

A.



B.



C.



D.



2. Identical $12\mu\text{C}$ charges are placed at the ends of a metre stick.




What is the electric potential at point P at the 60 cm mark on the metre stick?

- A. $9.0 \times 10^4 \text{ V}$
- B. $3.8 \times 10^5 \text{ V}$
- C. $4.5 \times 10^5 \text{ V}$
- D. $9.8 \times 10^5 \text{ V}$

A

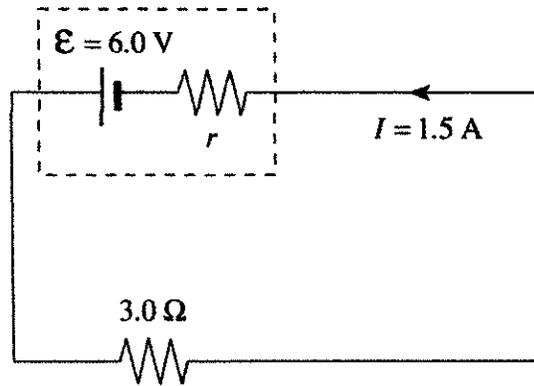
3. What is the internal resistance of the battery if it delivers 1.5 A when connected to a $3.0\ \Omega$ external load?



- A. $1.0\ \Omega$
- B. $3.0\ \Omega$
- C. $4.0\ \Omega$
- D. $7.0\ \Omega$


A

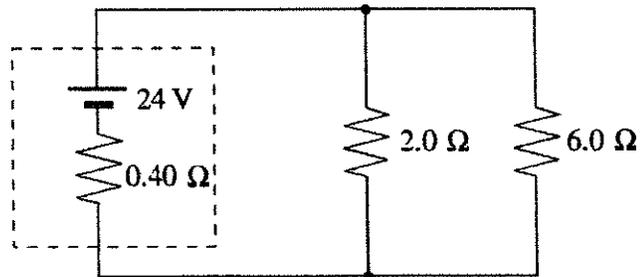4. In the circuit below, what is the current through the $2.0\ \Omega$ resistor?



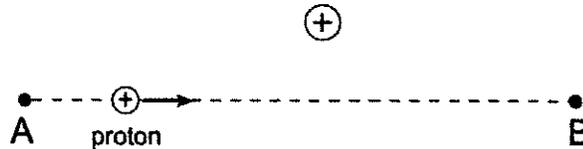- A. 9.5 A
- B. 10 A
- C. 12 A
- D. 13 A

- C 5. A proton is made to travel in a straight line near a fixed positively charged object as shown in the diagram below. What is happening to the proton's electric potential energy as it travels from A to B?




- A. It is increasing.
- B. It is decreasing.
- C. It is increasing then decreasing.
- D. It is decreasing then increasing.

- B 6. The terminal voltage of a battery is always less than the emf of a battery when supplying current in a circuit because of a voltage drop due to

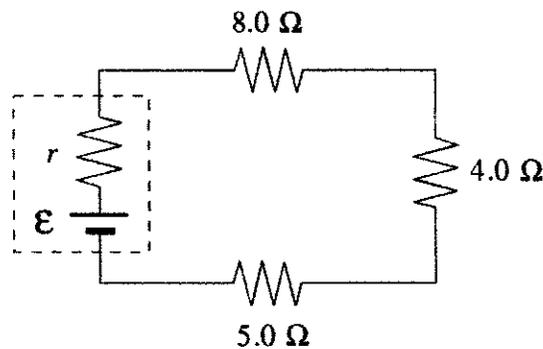- A. the terminal connections.
- B. the battery's internal resistance.
- C. heating of resistors in the circuit.
- D. heating of the wires in the circuit.

- A 7. When a resistor is added in parallel with the $4.0\ \Omega$ resistor in the circuit shown below, what happens to the voltage across the $5.0\ \Omega$ resistor and to the terminal voltage of the battery?




	VOLTAGE ACROSS $5.0\ \Omega$	TERMINAL VOLTAGE
A.	increases	decreases
B.	increases	increases
C.	decreases	decreases
D.	decreases	increases


①

8. Which diagram best illustrates the electric field between oppositely charged parallel plates?


A.

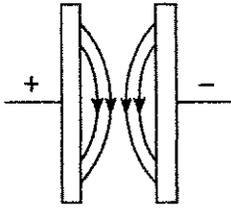


B.

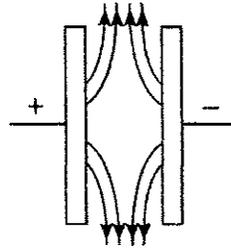

C.

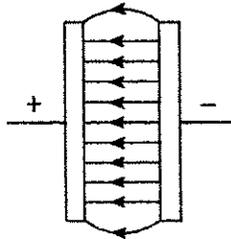


D.

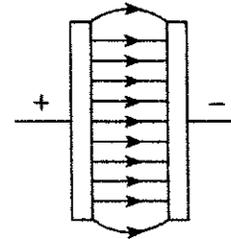

A

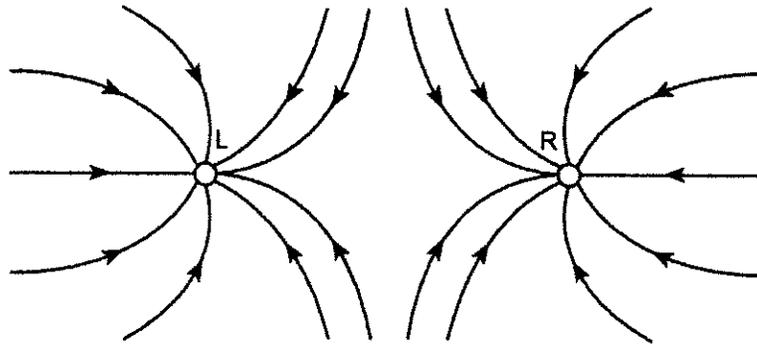9. The diagram shows the electric field lines near two point charges, L and R. Identify the polarity of these point charges.



	POLARITY OF L	POLARITY OF R
A.	Negative	Negative
B.	Negative	Positive
C.	Positive	Negative
D.	Positive	Positive

A

10. An electron orbits a nucleus which carries a charge of $+9.6 \times 10^{-19}$ C. If the electron's orbital radius is 2.0×10^{-10} m, what is its electric potential energy?

- A. -6.9×10^{-18} J
- B. -3.5×10^{-8} J
- C. 43 J
- D. 2.2×10^{11} J


C

11. Which household electrical appliance consumes the least energy in a typical month?

- A. Stove
- B. Dryer
- C. Clock
- D. Refrigerator

B

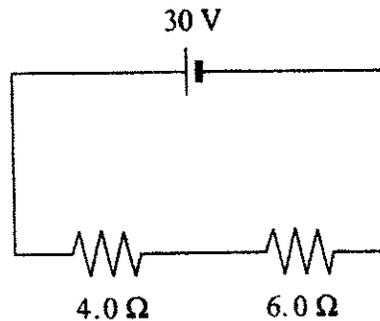12. What is the power output of the 6.0Ω resistor in the diagram?




- A. 36 W
- B. 54 W
- C. 90 W
- D. 150 W

B


13. A 12 V power supply is connected to an 8.0Ω resistor for 50 s. How much charge passes through the resistor?

- A. 1.9 C
- B. 75 C
- C. 900 C
- D. 4 800 C

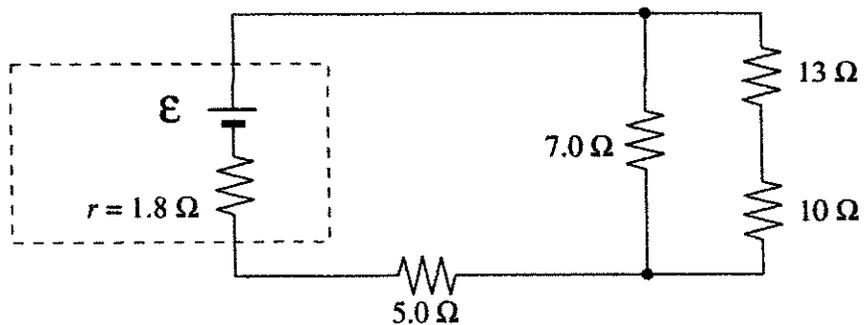(0.55 A) 14. The internal resistance of the battery shown in the circuit below dissipates 10 W of power.
Determine the current through the 13 Ω resistor. (7 marks)



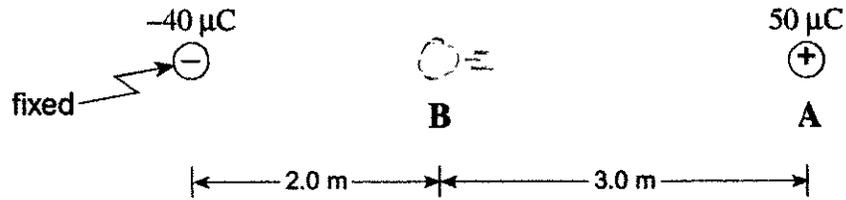15. A 1.0×10^{-3} kg styrofoam ball carrying $50 \mu\text{C}$ of charge is released from rest from position A as shown in the diagram below. ($1 \mu\text{C} = 1 \times 10^{-6}$ C)



(-5.4 J)

- a) Determine the change in electric potential energy, ΔE_p , of the ball as it moves from position A to position B. **(5 marks)**

$(1.0 \times 10^2 \frac{\text{m}}{\text{s}})$

- b) What is the speed of the ball as it reaches position B? ($v_i = 0$ at A) **(2 marks)**