


Answers

ELECTRICITY


1.

Which diagram best illustrates the electric field between oppositely charged parallel plates?


A.

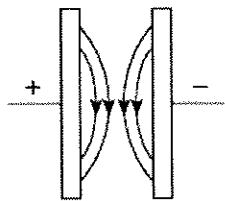


B.

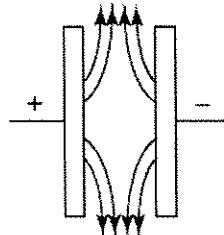

C.

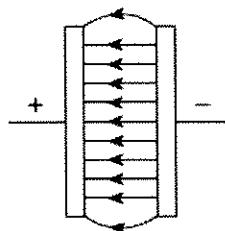


D.

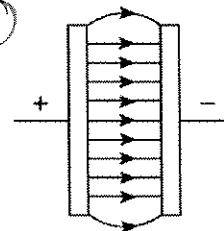

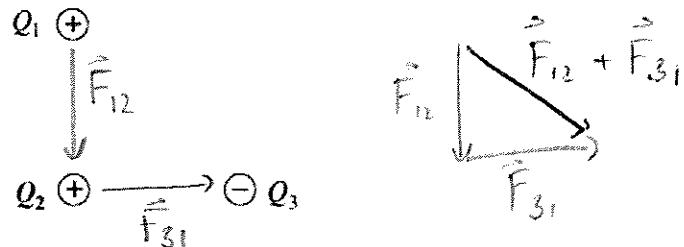2.


*• electric current flows
from + to - by convention*

Three charges of identical magnitude are arranged as shown.



What is the direction of the electric force on Q_2 ?


A.

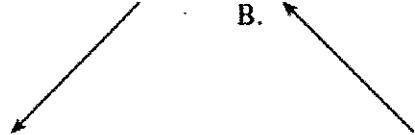

B.



C.

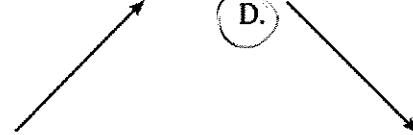

D.


3.

$$12 \times 10^{-6} C$$

$$r = 1.0 \text{ m}$$

$$V = \frac{kq}{r}$$

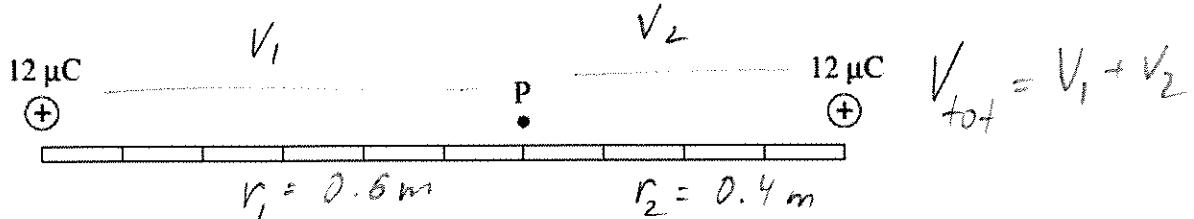Identical $12 \mu\text{C}$ charges are placed at the ends of a metre stick.



What is the electric potential at point P at the 60 cm mark on the metre stick?

A. $9.0 \times 10^4 \text{ V}$

B. $3.8 \times 10^5 \text{ V}$

C. $4.5 \times 10^5 \text{ V}$

D. $9.8 \times 10^5 \text{ V}$


$$V_{tot} = \frac{(9.00 \times 10^9)(12 \times 10^{-6})}{0.6} + \frac{(9.00 \times 10^9)(12 \times 10^{-6})}{0.4}$$

$$V_{tot} = 450,000 \text{ V}$$

$$V_{tot} = 4.5 \times 10^5 \text{ V}$$

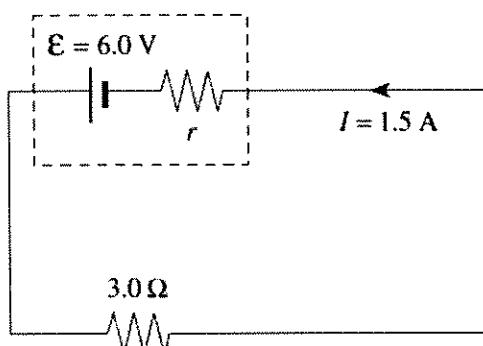4.

What is the internal resistance of the battery if it delivers 1.5 A when connected to a 3.0Ω external load?



$$\begin{aligned} V_{term} &= IR \\ &= (1.5)(3.0) \\ &= 4.5 \text{ V} \end{aligned}$$

- A. 1.0Ω
B. 3.0Ω
C. 4.0Ω
D. 7.0Ω

$$V_{term} = E - Ir$$

$$r = \frac{-V_{term} + E}{I}$$

$$r = \frac{-4.5 + 6.0}{1.5}$$

$$\underline{r = 1.0 \Omega}$$


$$R_{eq} = R_{loop} + r$$

5. $= 1.5 + 0.40$
 $\approx 1.9 \Omega$

$$\frac{1}{R_{loop}} = \frac{1}{2} + \frac{1}{6}$$

$$\frac{1}{R_{loop}} = \frac{4}{6} \rightarrow R_{loop} = \frac{3}{2} \Omega$$

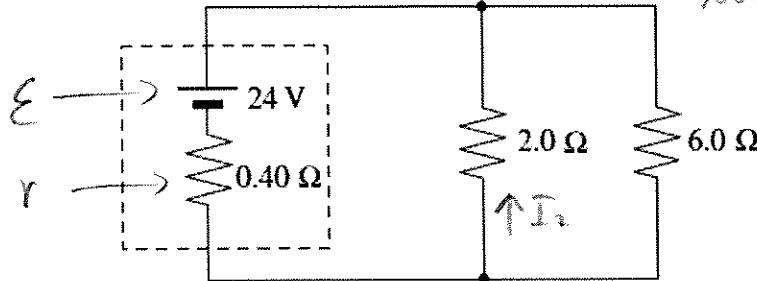In the circuit below, what is the current through the 2.0Ω resistor?



- A. 9.5 A
 B. 10 A
 C. 12 A
 D. 13 A

$$I = \frac{V}{R_{eq}} = \frac{E}{R_{eq}}$$

$$= \frac{24}{1.9}$$

$$\approx 12.6316 A$$

$$V_{term} = E - Ir$$

$$= 24 - (12.6316)(0.40)$$


$$\approx 18.9474 V$$

$$I_2 = \frac{V_{term}}{R_2}$$

$$= \frac{18.9474}{2.0} \approx 9.4737 A$$

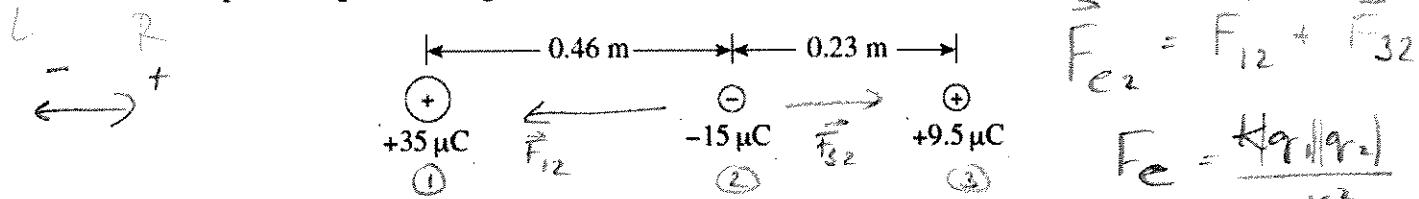6.

Three point charges are arranged as shown below.



What are the magnitude and direction of the electric force on the $-15 \mu C$ charge due to the other two point charges?

| MAGNITUDE OF ELECTRIC FORCE | DIRECTION OF ELECTRIC FORCE |
|-----------------------------|-----------------------------|
| A. 1.9 N ✓ | right ✓ |
| B. 1.9 N ✓ | left |
| C. 47 N | right ✓ |
| D. 47 N | left |

$$\vec{F}_{12} = -\frac{(9.00 \times 10^9)(35 \times 10^{-6})(15 \times 10^{-6})}{0.46^2}$$

$$\approx -22.3299 N$$

$$\vec{F}_{32} = \frac{(9.00 \times 10^9)(15 \times 10^{-6})(9.5 \times 10^{-6})}{0.23^2}$$

$$\approx 24.2439 N$$


$$F = -22.3299 + 24.2439$$

$$F \approx 1.9 N$$

positive \Rightarrow right


$$(A)$$

7.

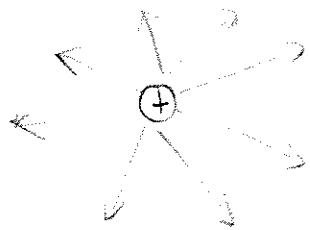


the greater the r,
the weaker the field

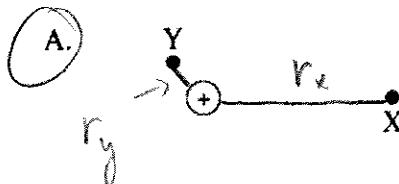Each diagram shows two points X and Y in the electric field near a positive charge.
In which case is the difference in the magnitudes of the electric field strengths for the
two points greatest? \rightarrow greatest difference in "r"




$$r_y \ll r_x$$

B.

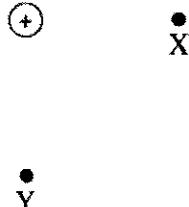

C.

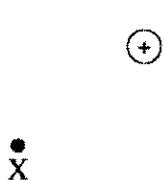

D.




8.

- What is the change in potential energy of a $6.0 \mu\text{C}$ charge when it is moved 3.0 m closer to a $45 \mu\text{C}$ charge as shown?

$$EPE = E_p = \frac{kq_1 q_2}{r}$$

$$\Delta EPE = EPE_f - EPE_i$$

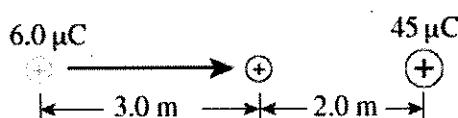- A. 0.49 J
 B. 0.73 J
 C. 1.2 J
 D. 1.7 J



$$! r_i = 2.0 + 3.0 = 5.0 \text{ m}$$

$$\Delta EPE = \frac{(9.00 \times 10^9)(6.0 \times 10^{-6})(45 \times 10^{-6})}{2.0} - \frac{(9.00 \times 10^9)(6.0 \times 10^{-6})(45 \times 10^{-6})}{5.0}$$

$$= 1.215 - 0.4860$$

$$= \underline{\underline{0.729 \text{ J}}}$$


$$m_e = 9.11 \times 10^{-31} \text{ kg}$$

$$q_e = -1.6 \times 10^{-19} \text{ C}$$

* The direction of an electric field is determined by its effect on a positive particle.

An electron travelling at $1.4 \times 10^7 \text{ m/s}$ enters the region between two charged parallel plates as shown.

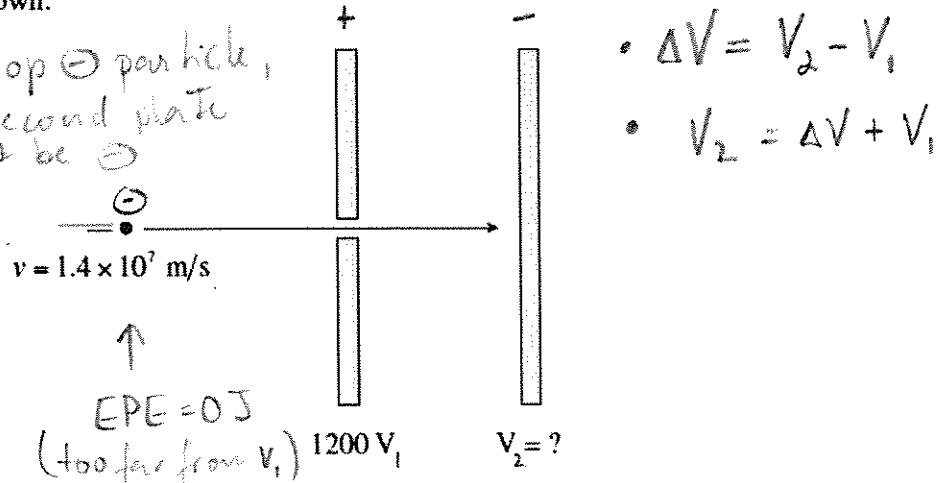- to stop Θ particle, the second plate must be Θ



$$\Delta V = V_2 - V_1$$

$$V_2 = \Delta V + V_1$$

What voltage applied to the second plate would result in the electron just reaching this plate ($v_f = 0$ at second plate) and what is the direction of the electric field between the plates?

| VOLTAGE APPLIED TO SECOND PLATE | DIRECTION OF E-FIELD * |
|---------------------------------|------------------------|
| A. 640 V ✓ | right ✓ |
| B. 640 V ✓ | left |
| C. 1800 V | right ✓ |
| D. 1800 V | left |

positive particle would be attracted to the second plate

• All KE goes into EPE \rightarrow ($E_i = E_f$)

$$|\Delta KE| = |\Delta EPE| \quad \text{and} \quad \Delta V = \frac{\Delta EPE}{q} = \frac{|\Delta KE|}{q}$$

$$\Delta KE = KE_f - KE_i$$

$$= 0 - \frac{1}{2}(9.11 \times 10^{-31})(1.4 \times 10^7)^2$$

$$= -8.9278 \times 10^{-17} \text{ J}$$


$$\Rightarrow \Delta EPE = +8.9278 \times 10^{-17} \text{ J}$$

$$\Delta V = \frac{8.9278 \times 10^{-17}}{-1.6 \times 10^{-19}} = -557.9875 \text{ V}$$

$$\begin{aligned} V_2 &= -557.9875 + 1200 \\ &= 642.0125 \\ &\approx 6.40 \times 10^2 \text{ V} \end{aligned}$$

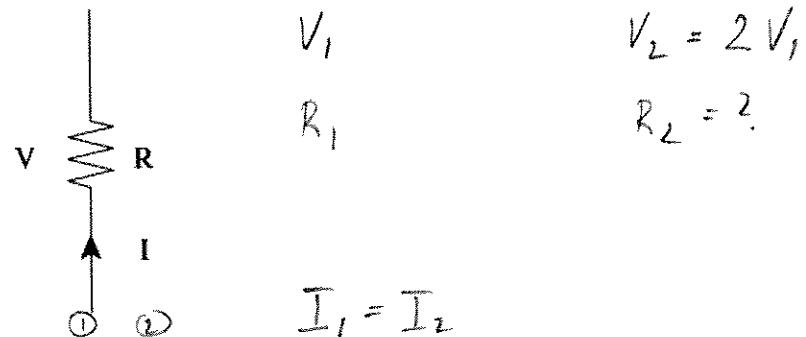10.

Consider the circuit element shown below.



The voltage across the resistor increases from V to $2V$. The current remains the same. By what factor has the resistance changed?

- A. $\frac{1}{4}$
B. $\frac{1}{2}$


- C. 2
D. 4

$$R_1 = \frac{V_1}{I_1}$$

$$R_2 = \frac{V_2}{I_2} = \frac{2V_1}{I_1} = 2 \cdot \frac{V_1}{I_1} = 2 \cdot R_1$$

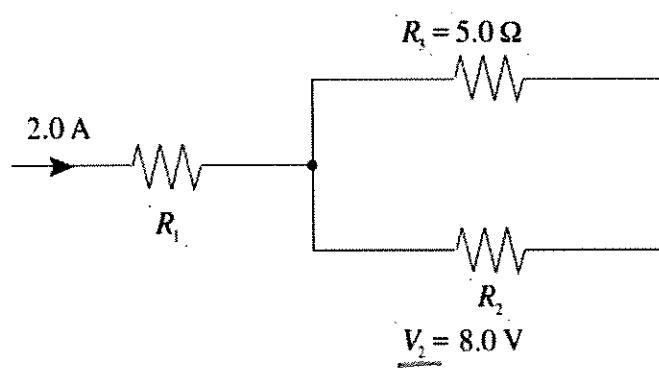11.

A current of 2.0 A flows through resistor R_1 as shown below.



R_3 and R_2
are in parallel
 $\Rightarrow V_3 = V_2$

What is the current flowing through the 5.0Ω resistor? (R_3)

- A. 0.40 A
B. 1.0 A
C. 1.2 A
D. 1.6 A

$$I_3 = \frac{V_3}{R_3} = \frac{V_2}{R_3}$$

$$= \frac{8.0}{5.0}$$

$$\underline{\underline{= 1.6\text{ V}}}$$

12.

An electric motor is being supplied with 4.2 A of current at 120 V. The resistance of the motor is 8.0Ω . How much power is the motor dissipating as heat?

- A. 15 W
- B. 1.4×10^2 W
- C. 5.0×10^2 W
- D. 1.8×10^3 W

$$P_{\text{lost}} = I \cdot V_{\text{lost}}$$

$$= (4.2)(33.6)$$

$$= 141.12 \text{ W}$$


$$\underline{\underline{= 1.4 \times 10^2 \text{ W}}}$$

$$\begin{aligned}V_{\text{lost}} &= Ir \\&= (4.2)(8.0) \\&= 33.6 \text{ V}\end{aligned}$$

internal resistance
↓

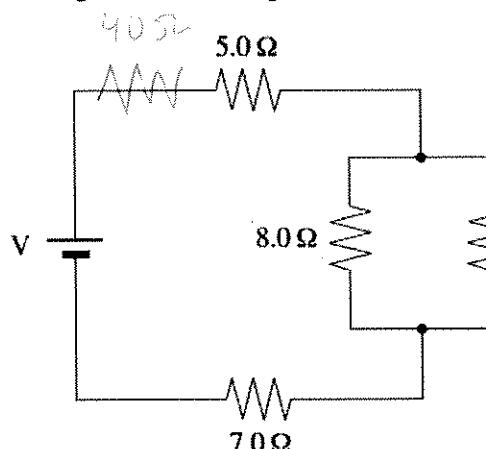13.

A power source is providing a constant voltage V to the circuit shown below.



- adding a resistor in series will increase R_{eq}
- adding a resistor in parallel will decrease R_{eq}

If a 4.0Ω resistor is added to the circuit in series with the 5.0Ω what happens to the equivalent resistance of the circuit and the current through the 7.0Ω resistor?

| | EQUIVALENT RESISTANCE OF THE CIRCUIT | CURRENT THROUGH 7.0Ω RESISTOR |
|----|--------------------------------------|---------------------------------------|
| A. | increases ✓ | decreases ✓ |
| B. | decreases | increases |
| C. | increases ✓ | increases |
| D. | decreases | decreases ✓ |

$R_{\text{eq}} \uparrow$


V is constant

$I = \frac{V}{R} \Rightarrow \frac{V}{R \uparrow} \Rightarrow I \downarrow$ (R and I are inversely proportional).

- both particles are \oplus
- \rightarrow they repel each other
- 14. \rightarrow they will stop when their KE transfers into EPE

Alpha particles with a mass of 6.6×10^{-27} kg and a charge of 3.2×10^{-19} C are fired towards each other from a great distance.

$$m = 6.6 \times 10^{-27} \text{ kg}$$

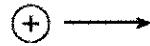

$$Q = 3.2 \times 10^{-19} \text{ C}$$

$$m = 6.6 \times 10^{-27} \text{ kg}$$



$$Q = 3.2 \times 10^{-19} \text{ C}$$

$$\bullet -\Delta KE = \Delta EPE$$

- a) If they each have a speed of 2.5×10^6 m/s to start with, what will be their minimum separation distance? (4 marks)

$$EPE = E_p = \frac{kq_1q_2}{r} \rightarrow r = \frac{kq_1q_2}{EPE} = \frac{(9.00 \times 10^9)(3.2 \times 10^{-19})(3.2 \times 10^{-19})}{2 \left[\frac{1}{2} (6.6 \times 10^{-27})(2.5 \times 10^6)^2 \right]}$$

two particles

$$r = 2.2 \times 10^{-14} \text{ m}$$

\therefore The minimum separation distance is 2.2×10^{-14} m.

- b) Using energy principles, explain why the particles do not come any closer than this minimum separation distance. (2 marks)

When all KE of the particles is transferred into EPE, they can't move any closer as they do not have any more energy left to overcome the repulsive electric force stemming from their like charge.


- Find r
- Find V_{term}

15.

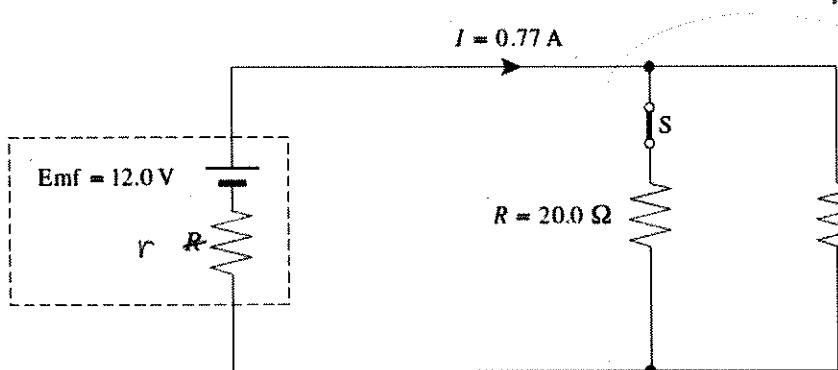3. (6 marks)

$$\mathcal{E}$$

A battery having an emf of 12.0 V is connected to the circuit as shown.



loop with resistors
in parallel

$$\frac{1}{R_{\text{loop}}} = \frac{1}{20.0} + \frac{1}{40.0}$$

$$\frac{1}{R_{\text{loop}}} = \frac{3}{40}$$

$$R_{\text{loop}} = \frac{40}{3} \Omega$$

What is the terminal voltage of the battery?

$$R_{\text{eq}} = r + R_{\text{loop}}$$

$$R_{\text{eq}} = \frac{\mathcal{E}}{I}$$

$$r = R_{\text{eq}} - R_{\text{loop}}$$

$$= 15.5844 - \frac{40}{3}$$

$$= \underline{\underline{2.25 \Omega}}$$

$$\frac{12.0}{0.77}$$

$$= 15.5844 \Omega$$

$$\begin{aligned} V_{\text{term}} &= \mathcal{E} - Ir \\ &= 12.0 - (0.77)(2.25) \\ &= 10.27 \text{ V} \end{aligned}$$

∴ The terminal voltage
 $1.03 \times 10^3 \text{ V}$.

Explain what happens to the terminal voltage of this battery when switch S is opened. \mathcal{E} is constant

\rightarrow no current through $R = 20.0 \Omega \Rightarrow R_{\text{eq}} = r + 40.0$

So R_{eq} is greater than before as the resistors are now in series only. $R_{\text{eq}} \uparrow$ and \mathcal{E} is constant leads to $I \downarrow$ \star . With less current going through the battery the voltage at the terminals will increase because (Ir) decreases and \mathcal{E} is constant


* $I = \frac{\mathcal{E}}{R_{\text{eq}}}$ $\rightarrow I_f = \frac{\mathcal{E}}{R_{\text{eq}}}$ \rightarrow greater R_{eq} yields smaller I
 $I_f < I_i$ because $R_{\text{eq}} < R_{\text{eq}i}$
 V_{term} increases

$$\bullet \vec{F}_1 = \vec{F}_{21} + \vec{F}_{31}$$

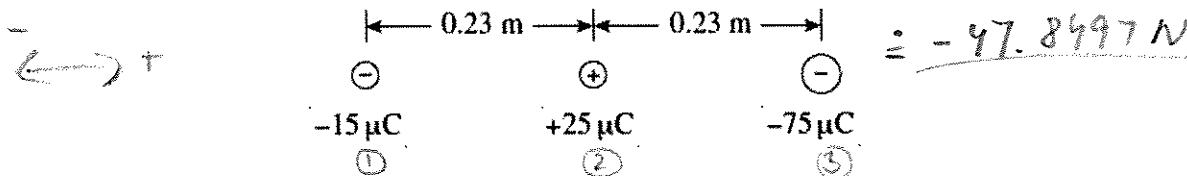16. $= 15.9499 \text{ N}$

positive \Rightarrow Right

Three point charges are arranged as shown below.




What are the magnitude and direction of the electric force on the $-15 \mu\text{C}$ charge due to the other two point charges?

| MAGNITUDE OF ELECTRIC FORCE | DIRECTION OF ELECTRIC FORCE |
|-----------------------------|-----------------------------|
| A. 16 N ✓ | Right ✓ |
| B. 16 N ✓ | Left |
| C. 110 N | Right |
| D. 110 N | Left |

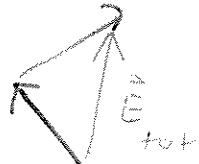17.

Two equally charged particles are placed close together as shown below.




Recall: the test particle
is always \oplus

Which of the following shows the net electric field due to these two particles at point R?



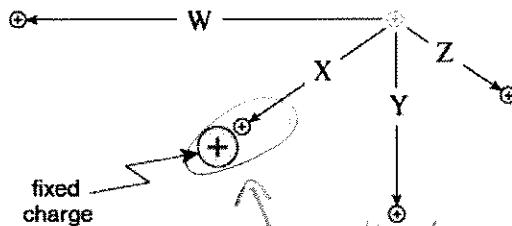18.

- A small test charge is moved to several different locations near a larger fixed charge as shown.



Which change in position of the smaller charge would require the most work?

$$W = \Delta EPE$$

- A. W
- B. X
- C. Y
- D. Z

$$EPE = \frac{kq_1q_2}{r}$$

→ the smaller the r,
the greater the EPE

19.


A proton initially held at rest 2.0 m away from a fixed $25 \mu\text{C}$ charge is released.

The proton accelerates to the right as shown.

$$\bullet N_i = 0 \text{ m/s}$$

$$\cancel{\bullet} KE_i = 0 \text{ J}$$
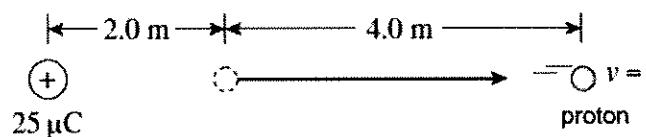
$$\bullet m = 1.67 \times 10^{-27} \text{ kg}$$



$$\bullet KE_i + EPE_i = KE_f + EPE_f$$

$$0 + EPE_i = \frac{1}{2}mv^2 + EPE_f$$

$$\rightarrow N = \sqrt{\frac{EPE_i - EPE_f}{\frac{1}{2}m}}$$

What is the speed of the proton when it is 6.0 m away from the $25 \mu\text{C}$ charge?

- A. $2.7 \times 10^6 \text{ m/s}$
- B. $3.3 \times 10^6 \text{ m/s}$
- C. $3.8 \times 10^6 \text{ m/s}$
- D. $4.6 \times 10^6 \text{ m/s}$

$$(9 \times 10^9)(25 \times 10^{-6})(1.6 \times 10^{-19}) \quad (9.00 \times 10^9)(25 \times 10^{-6})(1.6 \times 10^{-19})$$

2.0

6.0

$$\frac{1}{2}(1.67 \times 10^{-27})$$

$$N = \sqrt{\frac{(9 \times 10^9)(25 \times 10^{-6})(1.6 \times 10^{-19})}{2.0}} \quad \frac{(9.00 \times 10^9)(25 \times 10^{-6})(1.6 \times 10^{-19})}{6.0}$$

$$N = 3,790,944 \text{ m/s}$$


$$v = 3.8 \times 10^6 \text{ m/s}$$

$$20. \frac{1}{R_{loop}} = \frac{1}{25.0} + \frac{1}{30.0} \rightarrow R_{loop} = 13.6364 \Omega$$

$$R_{loop} = 0.073 \quad \bullet R_{eq} = 15.0 + 10.0 + R_{loop} = 38.6364 \Omega$$

A 12.0 V power supply is connected to 4 resistors as shown.

$$\bullet V = R \cdot I$$

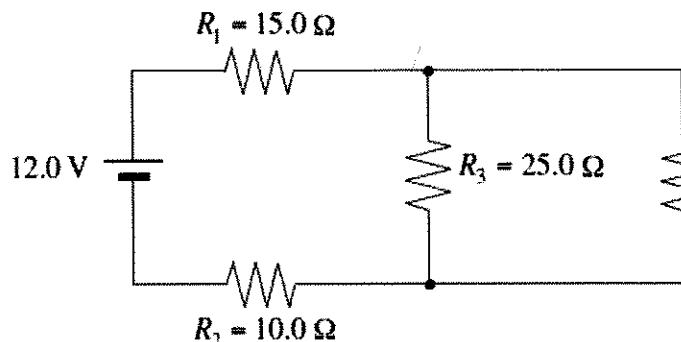

V_{loop}

$$\bullet I = \frac{V}{R_{eq}}$$

$$I = \frac{12.0}{38.6364}$$

$$= 0.3106 A$$

What is the potential difference, V_4 , across the 30.0Ω resistor?

- A. 2.12 V
- B. 4.24 V
- C. 9.32 V
- D. 12.0 V

$$\bullet V_2 = V_4 = V_{loop} \text{ (parallel resistors)}$$

$$\bullet V_{battery} = V_1 + V_2 + V_{loop}$$

$$\bullet V_1 = (15.0)(0.3106) \\ = 4.659 V$$

$$\bullet V_2 = (10.0)(0.3106) \\ = 3.106 V$$

$$\bullet V_{loop} = 12.0 - 4.659 - 3.106 \\ = 4.235 \\ = 4.24 V$$

21.

An electric motor is being supplied with 500 W of power at 120 V. The resistance of the motor is 8.0Ω . What current is being supplied to the motor?

- A. 4.2 A
- B. 7.9 A
- C. 15 A
- D. 63 A

$$P = IV \rightarrow I = \frac{P}{V}$$

$$I = \frac{500}{120}$$

$$I = 4.2 A$$


22.

a sphere is at rest

(5 marks)

A small sphere having a charge of $2.3 \mu\text{C}$ is suspended from a thread hanging between two charged plates as shown.

$$d = 0.031 \text{ m}$$

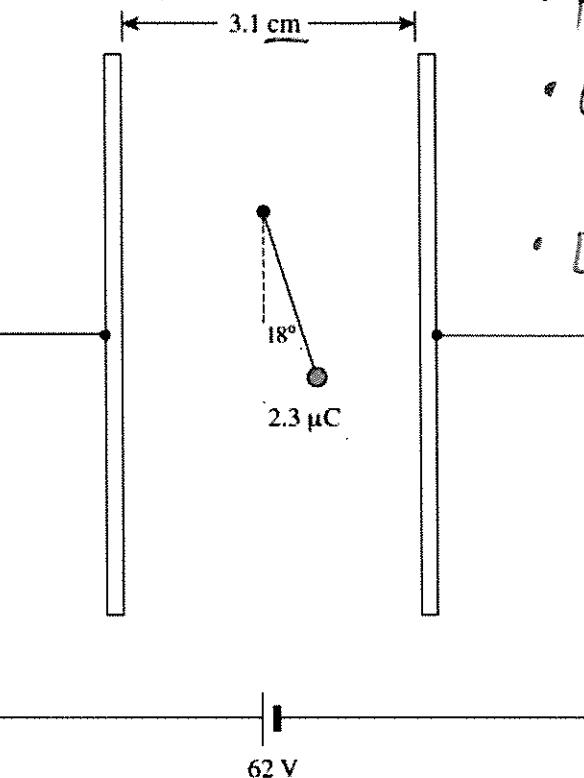

• parallel plates

$$\bullet E = \frac{\Delta V}{d} = \frac{62}{0.031} = 2000 \text{ N/C}$$

$$\bullet E = \frac{F}{q} \rightarrow F = Eq$$


$$\rightarrow \vec{F} = (2000)(2.3 \times 10^{-6}) \\ = 0.0046 \text{ N [R]}$$

What is the mass of the small sphere?

FBD:

$$F_{\text{net}} = 0 \text{ N}$$
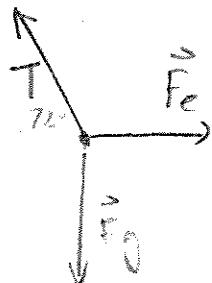
$$[0, 0] = [0, -mg] + [F_e, 0] + [-T_x, T_y]$$



$$\bullet 0 = 0 + F_e - T_x$$

$$\bullet 0 = -mg + T_y$$

$$0.0046 = T \cdot \cos 72^\circ$$

$$m = \frac{T_y}{g}$$

$$T = \frac{0.0046}{\cos 72^\circ}$$

$$= \frac{T \cdot \sin 72^\circ}{9.8}$$

$$T = 0.014885912 \text{ N}$$

$$= 0.001445 \text{ kg}$$

\therefore The mass of the sphere is $1.4 \times 10^{-3} \text{ kg}$.