

ELECTROMOTIVE FORCE—continued

1. Find the internal resistance in a 9.0V battery that supplies 0.40 A of electric current and its terminal voltage is 8.75 V.

2. A 9.0 V battery has internal resistance of $12\ \Omega$.


a) What is the potential difference across the battery's terminals when the battery supplies current of 50.mA?

b) What is the maximum current this battery can supply?

3. A battery has an emf of 12.0V and internal resistance of 0.15Ohms. What is the terminal voltage when the battery is connected to a 1.5 Ohm resistor?


"Special Case"

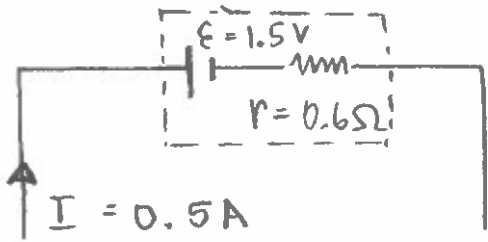4. A cell whose emf is 15V and internal resistance is 0.60Ω is charged by supplying a 0.5A current in the direction shown. What is the terminal voltage of the cell while being charged?




A Brief Review

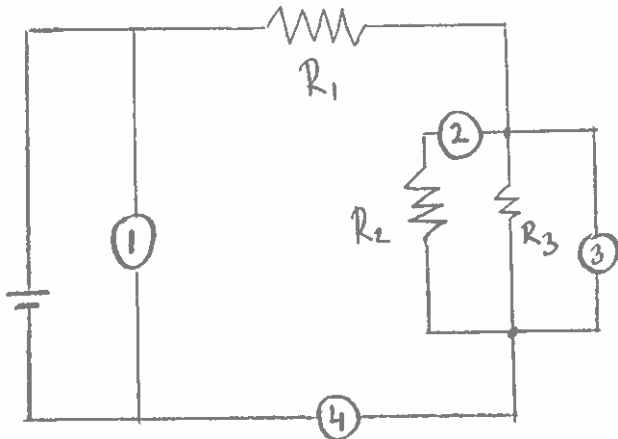1. The diagram below shows a circuit with four possible meter locations. In which locations should an ammeter and voltmeter be connected to correctly measure the current through R_1 and the voltage drop across R_2 ?



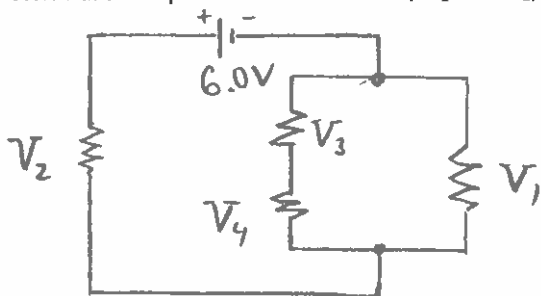
2. What are the potential differences, V_1 and V_2 , in the circuit shown below?



$$V_3 = 2V$$

$$V_4 = 3V$$

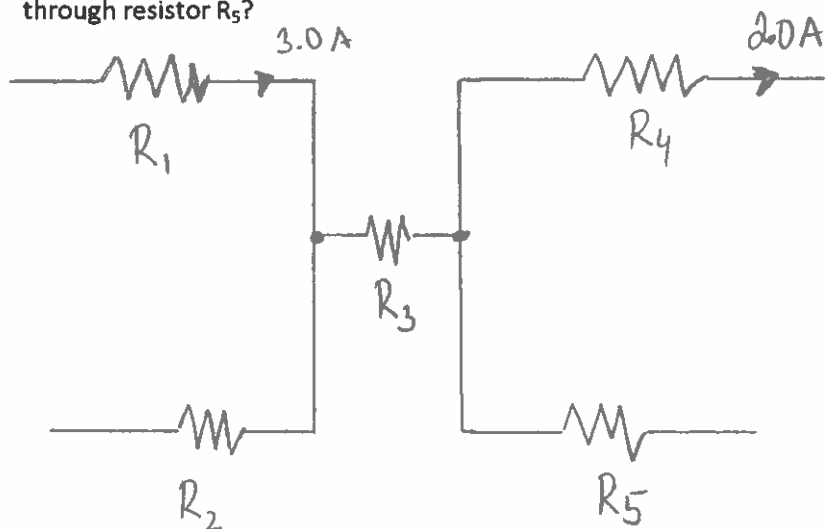
3. The diagram below shows part of an electrical circuit. What are the magnitude and direction of the current passing through resistor R_5 ?



4. A 12 V battery is connected to a 60Ω resistor. How much charge will flow through the resistor in 20 s ?

5. A 2.50 W device requires a 1.2 V to operate properly. A 1.45 V cell, with internal resistance r , is used to power this device. What value of r enables the cell to provide 1.20 V to the device?

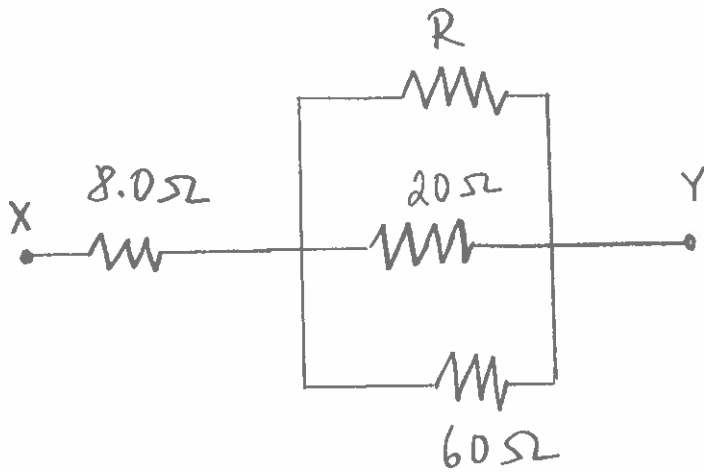6. The total resistance between X and Y is 14.0Ω . What is the value of R?



7. The current in the 8.00Ω resistor in the circuit below is 0.500 A . Find the current in the 20.00Ω resistor. **Justify each value by a calculation or Kirchoff's Rule.**

