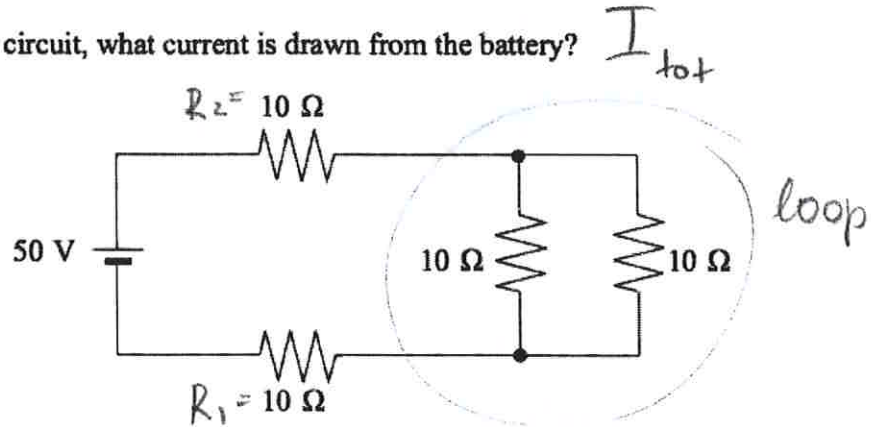


Ohm's Law, Resistance, Power and Kirchhoff's Laws

Examples

1.

In the following circuit, what current is drawn from the battery?



- A. 1.3 A
- B. 1.7 A
- C. 2.0 A
- D. 5.0 A

$$\begin{aligned}
 R_{eq} &= R_1 + R_2 + R_{loop} \\
 &= 10 + 10 + 5 \\
 &= \underline{25\ \Omega}
 \end{aligned}$$

$$I = \frac{V_{battery}}{R_{eq}}$$

R_{loop} :

$$\begin{aligned}
 \frac{1}{R_{loop}} &= \frac{1}{10} + \frac{1}{10} \\
 &= \frac{2}{10}
 \end{aligned}$$


$$R_{loop} = \frac{10}{2} = \underline{5.0\ \Omega}$$

$$I = \frac{50}{25}$$

$$\underline{\underline{I = 2.0\ A}}$$

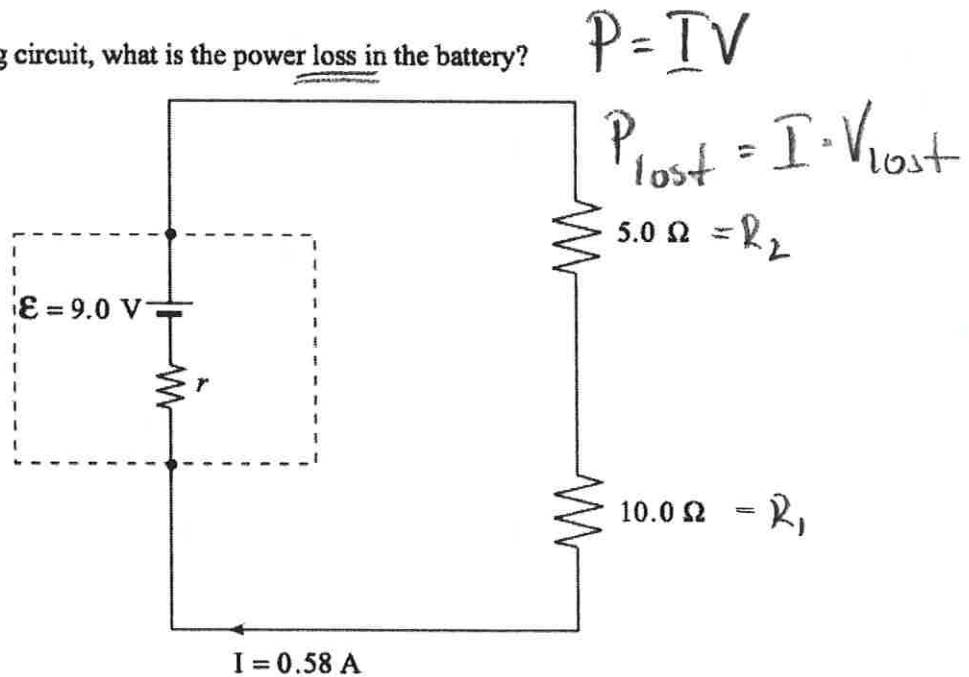2.

In the following circuit, what is the power loss in the battery?



- A. 0 W
- B. 0.17 W
- C. 5.0 W
- D. 5.2 W

$$V_{\text{lost}} = \mathcal{E} - V_{\text{term}}$$

$$V_{\text{lost}} = 9.0 - 8.7 \\ = \underline{0.3 \text{ V}}$$

$$V_{\text{term}} = \mathcal{E} - Ir$$


$$V_{\text{term}} = I(R_1 + R_2) \\ = (0.58)(15.0) \\ = 8.7 \text{ V}$$

$$P_{\text{lost}} = (0.58)(0.3) \\ = 0.174 \text{ W}$$

3.

In the circuit shown below, determine the current through the 5.0 Ω resistor.

(7 marks)

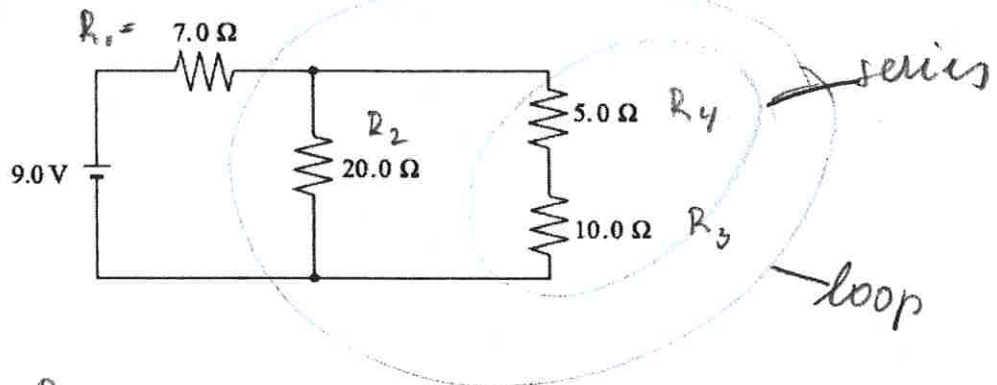

$$\bullet R_{eq} = R_1 + R_{loop}$$

$$R_{eq} = 7.0 + \frac{60}{7}$$

$$= 15.5714 \Omega$$

$$\bullet I_{tot} = \frac{V}{R_{eq}}$$

$$= \frac{9.0}{15.5714}$$

$$= 0.577982 \dots A$$

$$\bullet R_{loop} =$$

$$\frac{1}{R_{loop}} = \frac{1}{R_2} + \frac{1}{R_3 + R_4}$$

$$= \frac{1}{20} + \frac{1}{15}$$

$$= \frac{3+4}{60}$$

$$= \frac{7}{60} \rightarrow R_{loop} = \frac{60}{7} \Omega$$

$$\bullet V_{loop} = V_{battery} - V_1$$

$$= 9.0 - (0.577982)(7.0)$$





$$= 4.9541 V$$

$$\bullet V_{loop} = V_{series} \rightarrow I_{series} = I_4 = \frac{V_{series}}{R_{series}} = \frac{4.9541}{(5+10)} = 0.331$$

$$I = \frac{V}{R} \Rightarrow \text{large } I \Leftrightarrow \text{small } R$$

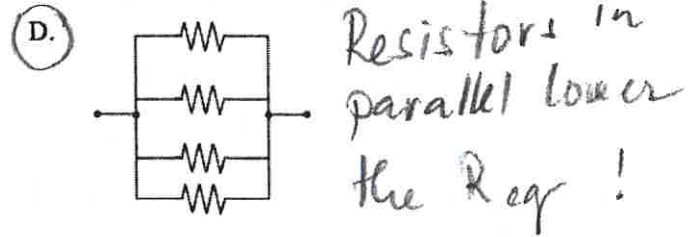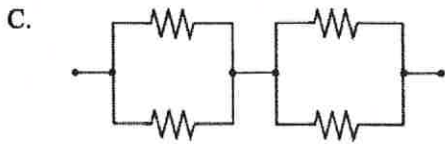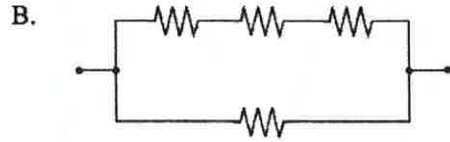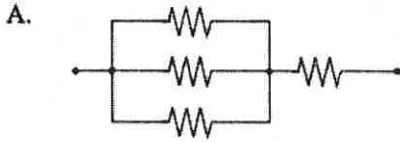
4.

Which of the following arrangements would draw the largest current when connected to a potential difference? All resistors have the same value.



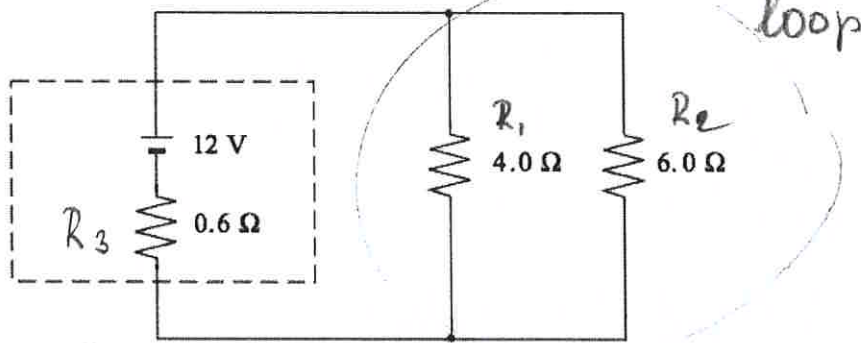5.

In the following circuit, what current flows through the 4.0Ω resistor?



- A. 2.4 A
- B. 2.6 A
- C. 3.0 A
- D. 4.0 A

② $R_{eq} = R_3 + R_{loop}$
 $R_{eq} = 0.6 + \frac{12}{5}$
 $= 3.0 \Omega$

① $\frac{1}{R_{loop}} = \frac{1}{4.0} + \frac{1}{6.0}$
 $\frac{1}{R_{loop}} = \frac{3+2}{12}$
 $R_{loop} = \frac{12}{5} \Omega$

⑤ $V_{loop} = V_1 = V_2$

⑥ $I_2 = \frac{V_2}{R_2}$
 $= \frac{9.6}{6.0}$


2.4 A

③ $I = \frac{V}{R_{eq}}$
 $= \frac{12}{3.0}$
 $= 4.0 A$

④ $V_{loop} = V_{battery} - V_3$
 $= 12.0 - (4.0)(0.6) = 9.6 V$

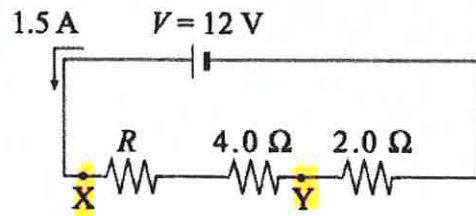6.

In the following circuit, what is the magnitude of the potential difference between X and Y?



- A. 3.0 V
- B. 6.0 V
- C. 9.0 V
- D. 12 V

$$\begin{aligned} R_{\text{eq}} &= \frac{V}{I} \\ &= \frac{12}{1.5} \\ &= 8.0\ \Omega \end{aligned}$$

$$\begin{aligned} R_{\text{eq}} &= R + 4.0 + 2.0 \\ \rightarrow R &= 8.0 - 4.0 - 2.0 \\ &= \underline{\underline{2.0\ \Omega}} \end{aligned}$$

$$\begin{aligned} V_{XY} &= I_{\text{tot}} \cdot R_{XY} \\ &= (1.5)(2.0 + 4.0) \\ &= \underline{\underline{9.0\text{ V}}} \end{aligned}$$